

20/03/2023

BEEE

① Independent Sources

both voltage and current don't depend on voltage or current else where in the circuit

② Dependent Sources



both voltage or current depends on voltage or current else where in circuit.

current
independent
sources

voltage
independent
source

current
dependent
sources

voltage
dependent
sources

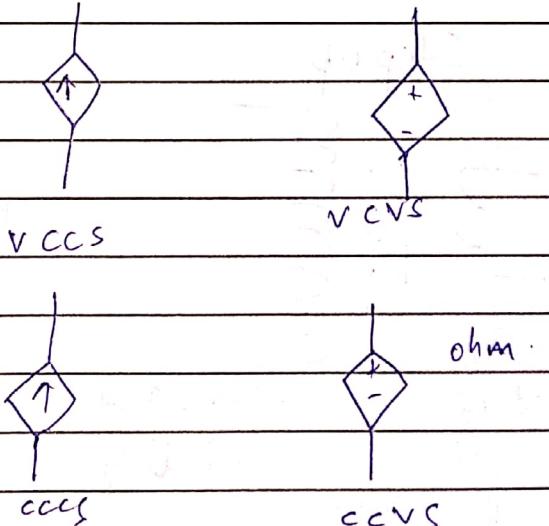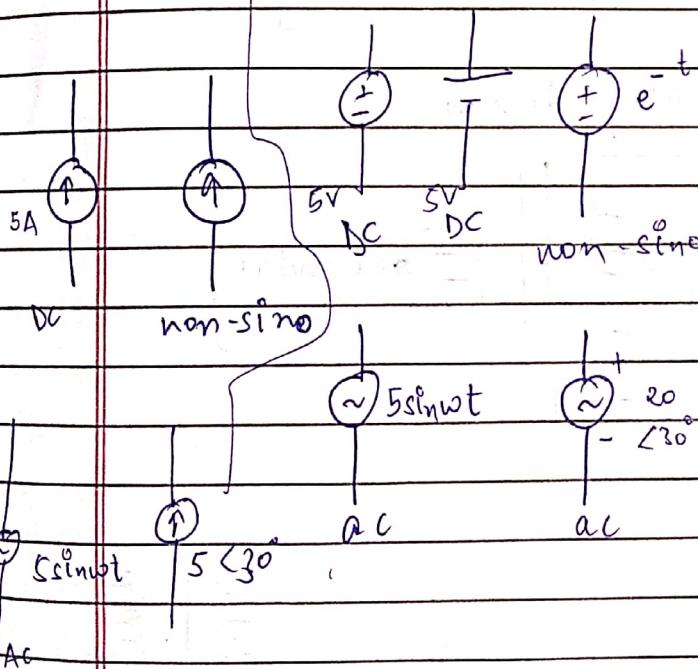

Q) Why AC is required over DC?



In AC flow of current changes its dirⁿ forward and backward periodically.

DC → it flows in a single dirⁿ steadily.

- # AC it has frequency loss over DC over transmission over long distance.
- # cheaper to generate.

TRANSFORMERS

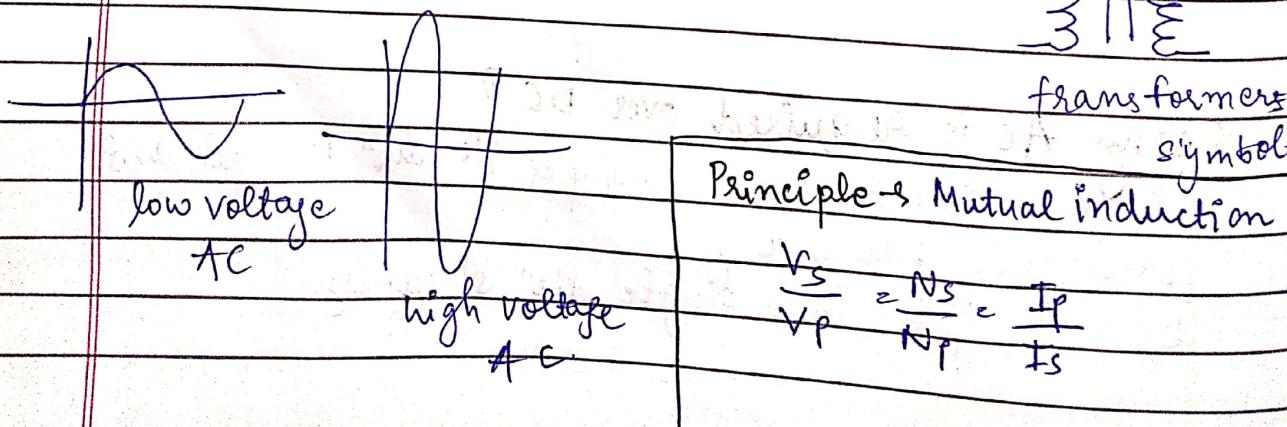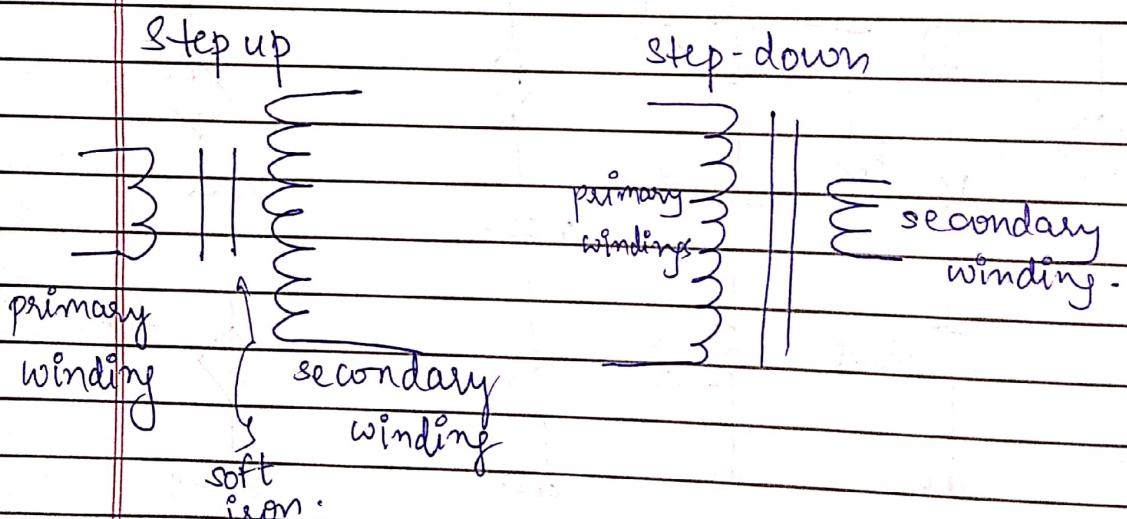- ① Voltage coming into the transformer from power source is primary voltage.
- ② That which is going to supply is secondary voltage.
- ③ For ex → doorbell 15 V operates, while power circuit carries 230 V - 100 V so this balance between input and output voltage is managed by step down transformer which reduces the voltage.




22/03/2013

classmate

Date _____

Page _____

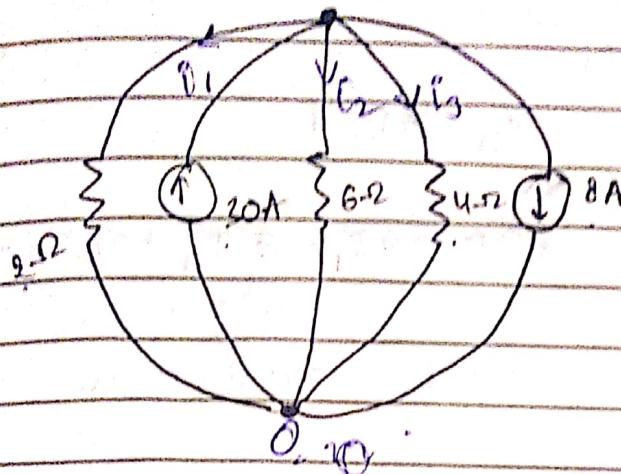V_{MAX}

find value of V.


$$\frac{V}{2} + \frac{V}{6} + \frac{V}{4} = 20$$

$$I_1 + I_2 + I_3 + 8 = 30$$

$$I_1 + I_2 + I_3 = 22$$

$$\frac{V}{2} + \frac{V}{6} + \frac{V}{4} = 22$$

$$V = 24 \text{ V}$$

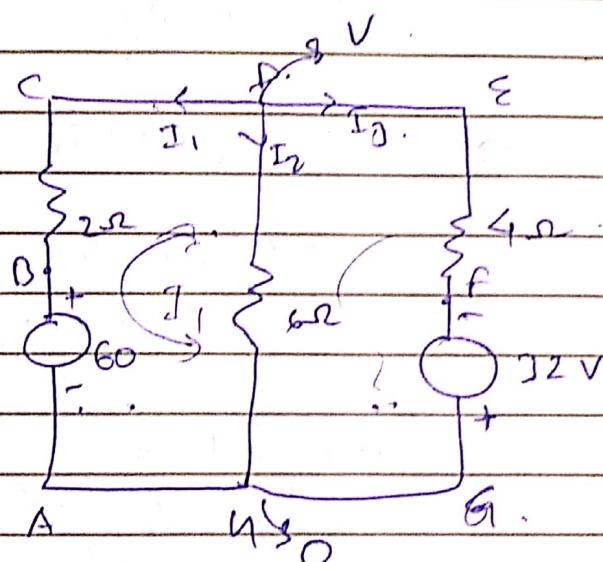
 $\therefore \text{through } 60\Omega \text{ m} = 4 \text{ A.}$

$$I_1 + I_2 + I_3 = 0$$

$$\frac{V - 60}{2} + \frac{V - 0}{6} + \frac{V + 32}{4} = 0.$$

$$-60 + 2I_1 + 6(I_1 - I_2) = 0 \quad -60 + 8I_1 - 6I_2 = 0$$

$$8I_1 - 6I_2 = 60$$

$$4I_2 - 32 + 6(I_2 - I_1) = 0. \quad 10I_2 - 32 - 6I_1 = 0.$$

$$60 + 8I_1$$

$$\frac{8}{8}$$

$$144$$

$$\frac{144}{8}$$

$$18$$

$$I_1 = 18$$

$$I_1 = \frac{60 + 6I_2}{8}$$

$$308 = 224$$

$$I_2 = 14$$

$$8 \times (60 + 6I_2) - 10I_2 = -32$$


$$8I_2 - 32 - 10I_2 = -32$$

$$-2I_2 = -32$$

$$I_2 = 16$$

$$180 + 18I_2 - 40I_2 = 128.$$

Q

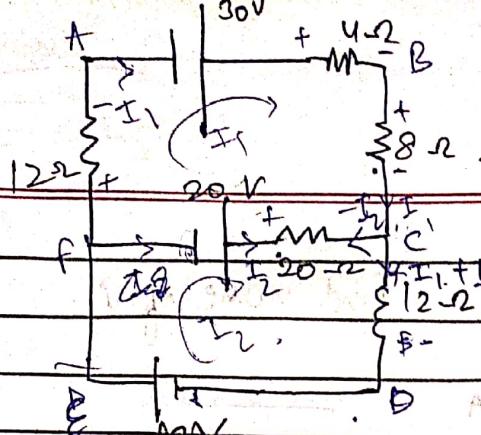

Q find the magnitude of

CLASSMATE

Date _____

Page _____

Q

In ABCf.

$$+30 = 4I_1 - 8I_2 + 20I_3 - 12I_4 \quad | :20$$

$$24I_1 - 20I_2 = 10 \quad | \cancel{20}$$

$$20 + -20I_2 + 12(I_1 + I_2) + 10 = 0$$

$$30 = 20I_2 + 12I_1 + 12I_2$$

$$\begin{aligned} 30 &= 42I_2 + 12I_1 \\ 60 &= 84I_2 + 24I_1 \\ 10 &= -20I_2 + 24I_1 \end{aligned}$$

$$30 = 32I_2 + 12I_1$$

$$60 = 64I_2 + 24I_1$$

$$10 = -20I_2 + 24I_1$$

$$50 = 84I_2$$


$$I_2 = 0.595$$

$$I_2 = 0.6$$

$$10 = -12 + 24I_1 \quad | \cancel{-12}$$


$$22 = 24I_1 \quad | :24$$

$$I_1 = 0.9$$

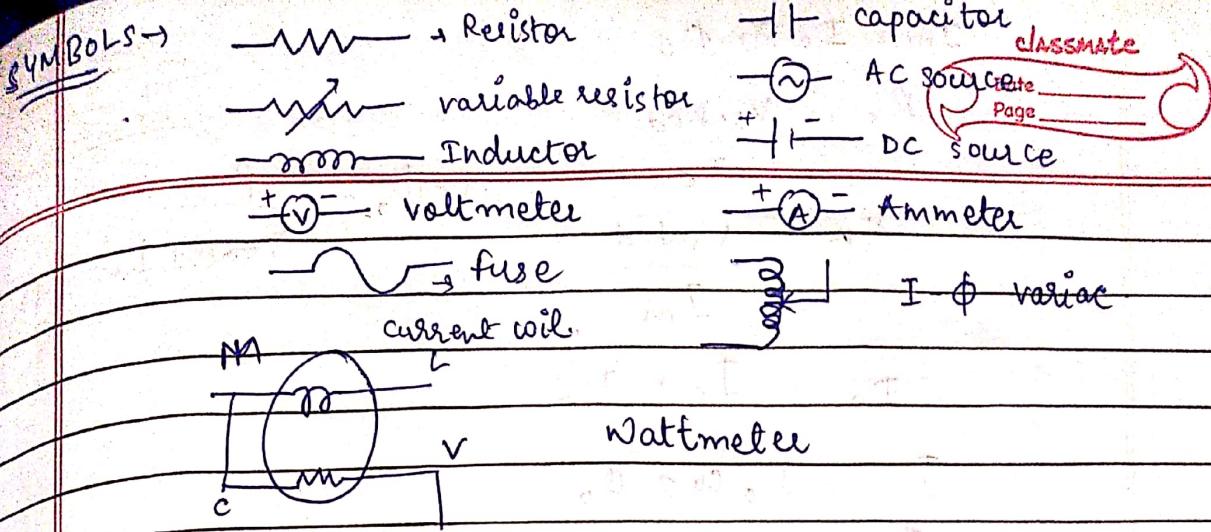


Wattmeter shows active power

AC circuit → three types of power

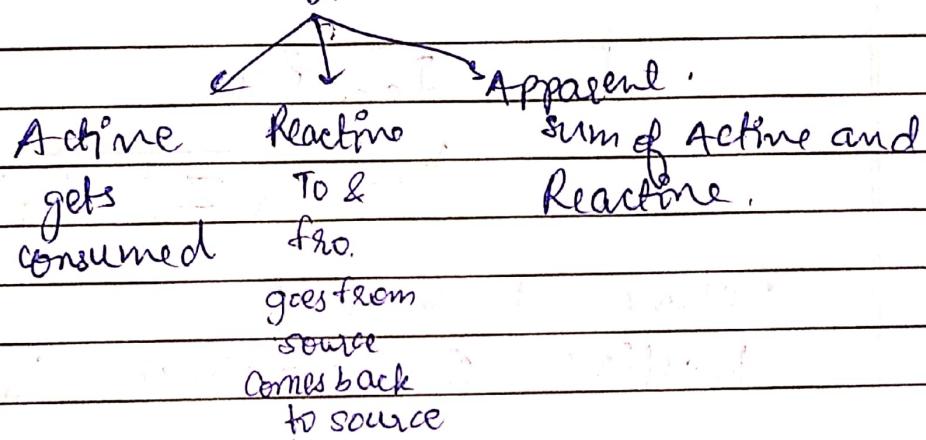

Transformer experiment

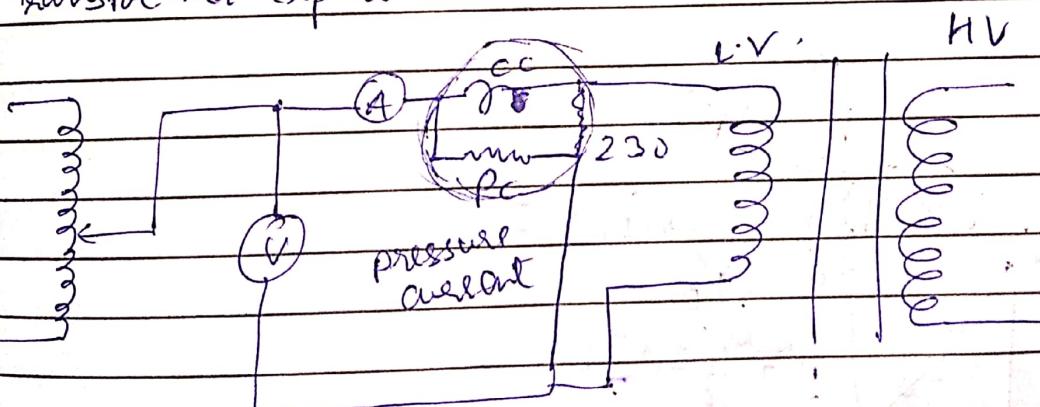

$$P_o = V_{\text{rated}} I_o \cos \phi_o$$

$$\cos \phi_o = \frac{P_o}{V_{\text{rated}} I_o}$$

$$P_c = I_o \cos \phi_o$$

$$I_m^2 = I_o \sin \phi_o$$

$$R_c = \frac{V_{rated}}{I_c}$$

$$\cos \phi_o = \frac{P}{I_o}$$

$$X_m = \frac{V_{rated}}{I_m}$$

$$V_{rated} = I_o X_m$$

$$T_o = I_c + T_m$$

$$I_c = I_o \cos \phi_o$$

$$I_m = I_o \sin \phi_o$$

$$Z_{sc} = \frac{V_{sc}}{I_{sc}}$$

$$P_{sc} = I_{sc}^2 R_{eq}$$


$$X_{eq} = \sqrt{Z_{sc}^2 - R_{eq}}$$

$$\text{Active} = P = V I \cos \phi$$

$$\text{Reactive} = Q = V I \sin \phi \quad V_{ar}, \text{ KVA}$$

$$S = \sqrt{P^2 + Q^2}$$

Q

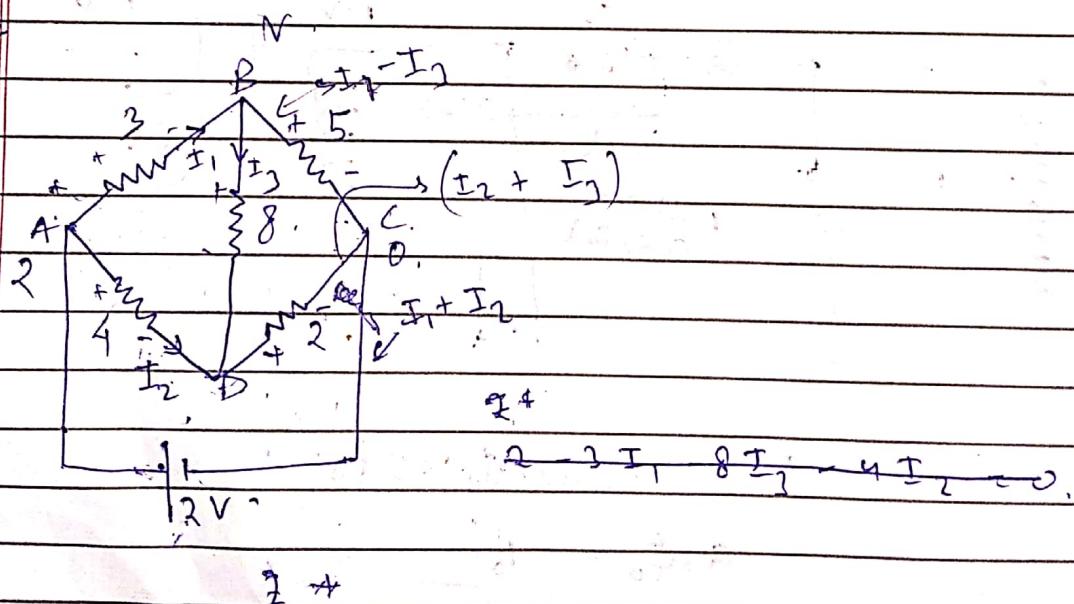

In A B D A

$$3I_1 + 8I_3 - 4I_2 = 0 \quad \text{--- (i)}$$

classmate

Date _____

Page _____

In B C D B

$$5(I_1 - I_2) - 2(I_2 + I_3) - 8I_3 = 0$$

$$5I_1 - 5I_2 - 2I_2 - 2I_3 - 8I_3 = 0$$

$$5I_1 - 15I_2 - 2I_3 = 0 \quad \text{--- (ii)}$$

A D C A

$$8 + 4I_2 + 2(I_1 + I_2) - 2 = 0$$

$$6I_2 + 2I_3 = 2 \quad \text{--- (iii)}$$


$$\begin{bmatrix} 3 & -4 & 8 \\ 5 & -2 & -10 \\ 0 & 6 & 2 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 2 \end{bmatrix}$$

$$3 \downarrow \quad 15I_1 - 45I_2 - 6I_3 = 0 \quad I_1 = 0.28$$

$$2I_3 + 6I_2 = 2 \quad I_2 = 0.314$$

$$I_3 = 0.53$$

$$15I_1 - 45I_2 = 2$$

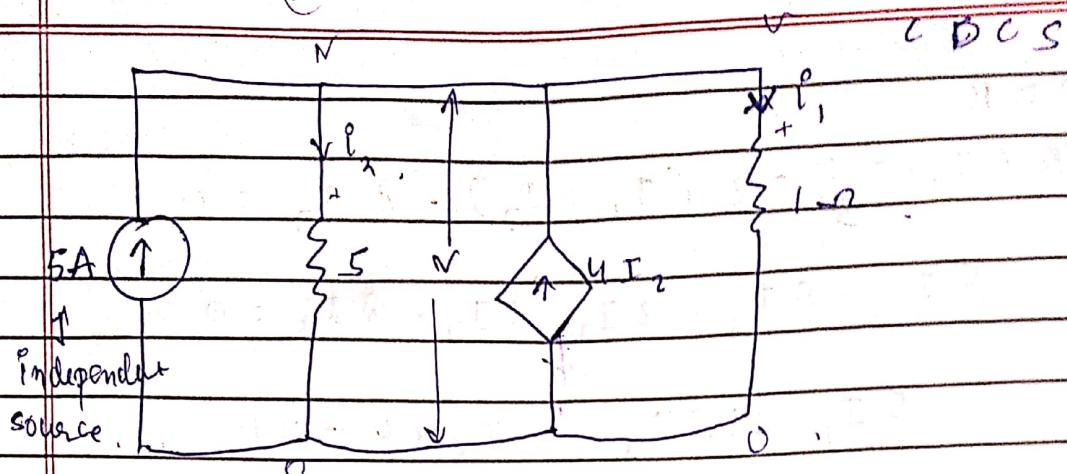

$$\dot{i}_1 + \dot{i}_2 = 5 + 4I_2$$

$$\dot{i}_1 - 3\dot{i}_2 = 5.$$

$$V - 3x \frac{V}{5} = 5$$


$$5V - 3V = 25$$

$$V = 12.5.$$

for solving a particular network
2 methods

Nodal Analysis $\rightarrow n = j - 1$

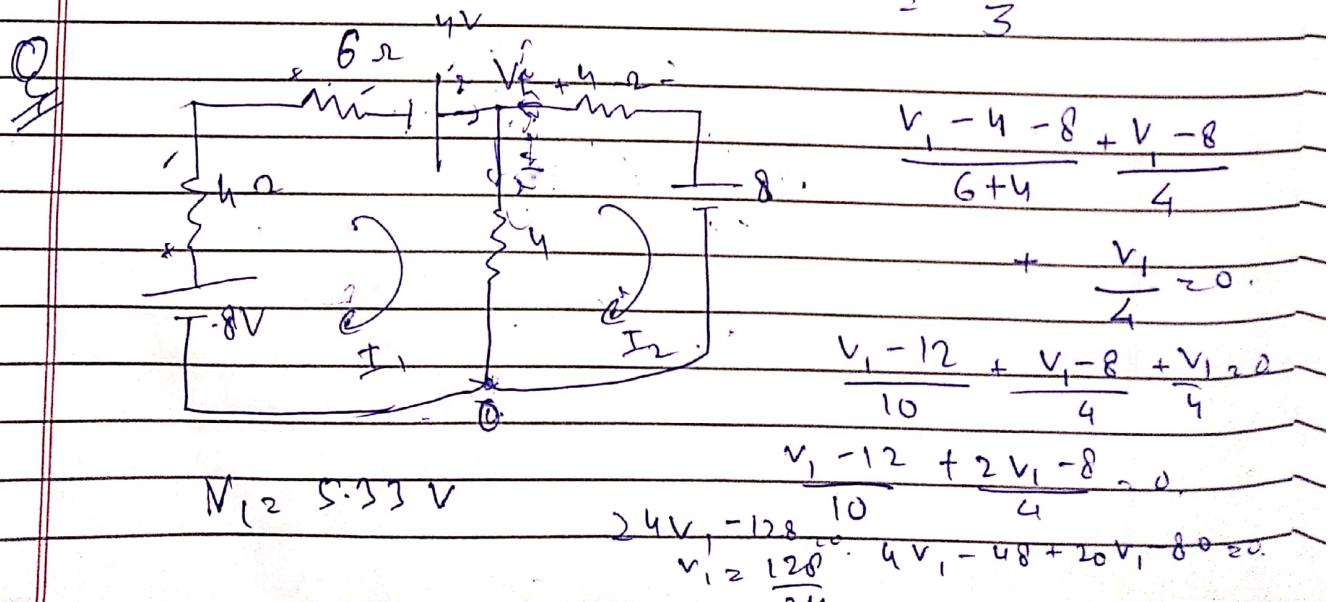Mesh Analysis $\rightarrow m = b - (j - 1) = 5 - (3 - 1) = 3$



$$-8 + 4I_1 + 6I_2 - 4 + 4(I_1 - I_2) \geq 0,$$

$$14I_1 - 4I_2 \geq 12.$$

$$28I_1 - 8I_2 \geq 24$$

$$4I_2 + 8 + (I_2 - I_1) \leq 0,$$

$$-4I_1 + 8I_2 \leq -8.$$

$$28I_1 - 8I_2 \geq 24$$


$$24I_1 = 16.$$


$$I_1 = 0.67.$$

$$18.76 - 8I_2 = 24$$

$$-8I_2 = 5.24$$

$$I_2 = -0.655$$

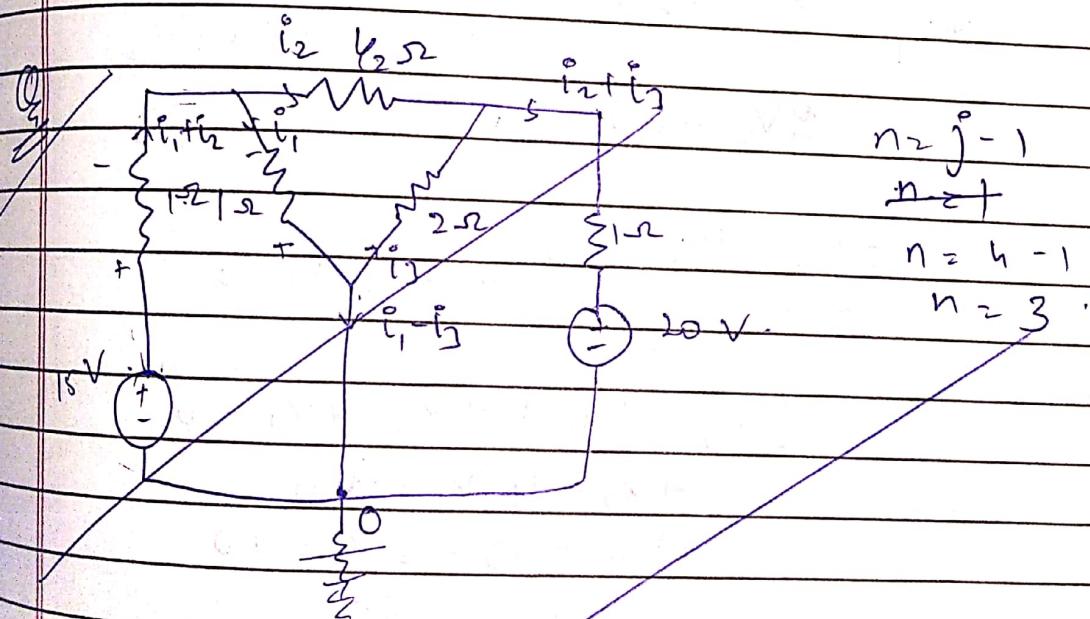

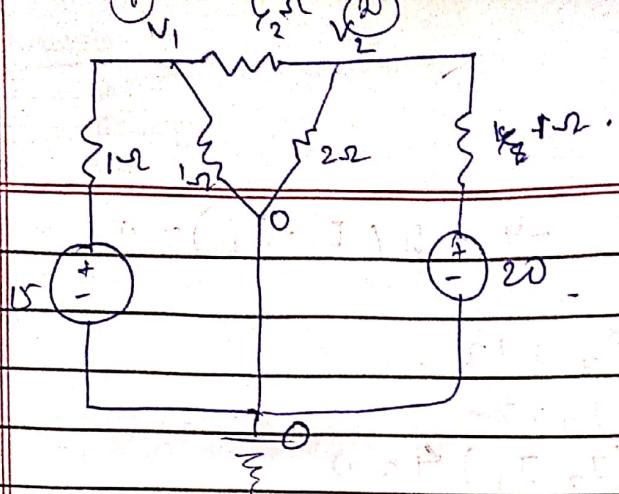

$$\frac{V_1 - 15}{1} + \frac{V_2 - 20}{1} + \frac{V_1 - 0}{1} = 0$$

$$\frac{V_1 - 15}{1} + \frac{V_1 - 0}{1} + \frac{V_1 - V_2}{1} = 0$$

$$\frac{V_2 - 20}{2} + \frac{V_2}{2} + \frac{V_2 - V_1}{4} = 0$$

$$4V_1 - 2V_2 = 15$$

$$4V_1 = 15 + 2V_2$$

$$4V_2 - 2V_1 = 20$$

$$\frac{2V_2 - 40 + V_2}{2} \rightarrow 2V_2 - 2V_1 = 20$$

$$3V_2 - 40 + 4V_2 - 4V_1 = 0$$

$$7V_2 - 4V_1 = 40$$

$$7V_2 - 15 - 2V_2 = 40$$

$$5V_2 = 55$$

$$V_2 = 11V$$

$$V_1 = 9.75V$$

$$V_1 = 15$$

$$7V_2 - 4V_1 = 40$$

$$3V_2 = 4V_1$$


$$V_1 = 9.75$$

m = b - (j-1)

classmate

Date _____

Page _____

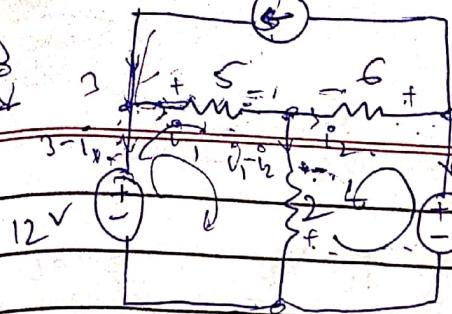

$$m = 6 - (4-1)$$

$$\Rightarrow 6 - 3 = 3$$

$$-5i_1 + 2(i_1 - i_2) + 12 = 0$$

$$(2 \times 6) - 6 - (i_1 - i_2) \times (-2) = 0$$

$$\cancel{-5i_1} - 5i_1 + 2i_1 - 2i_2 + 12 = 0$$

$$3i_1 + 2i_2 = 12$$

$$-12 + (I_1 + 3)5$$

$$6i_2 + i_1 - i_2 = 6$$

$$+ (I_1 - I_2)2 = 0$$

$$\Rightarrow i_1 + 5i_2 = 6$$

$$i_1 = 1.2$$

$$i_1 = 6 - 5i_2$$

$$i_2 = 0$$

$$6 + (I_2 - I_1)2 + (I_2 + 3)6 = 0 \quad 3(6 - 5i_2) + 2i_2 = 12 \quad 2.06$$

$$18 - 15i_2 + 2i_2 = 12$$

$$6 = 13i_2$$


$$i_2 = \frac{6}{13}$$

$$1.5$$

$$3i_1 + 12 = 12$$

$$3i_1 = 12 - 12$$

$$2$$

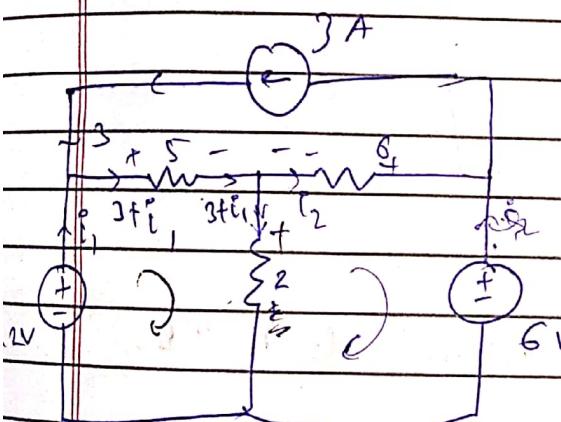

$$3i_1 = 12$$

$$-12 + (3 + i_1)5$$

$$+ (3 + i_1 - i_2) \times 2 = 0$$

$$-12 + (5 + 5i_1) + 6 + 2i_1 - 2i_2 = 0$$

$$5 + 8 + i_1 - 2i_2 = 0$$

$$4i_2 = -2i_1$$

$$2i_2 = -i_1$$

$$-i_2 \times 6 + 6 + (3i_2 - 3 - i_1) \times 2 = 0$$

$$-6i_2 + 6 + 2i_2 - 6 - 2i_1 = 0$$


$$-4i_1 = 0$$

THEVENIN'S THEOREM

classmate

Date _____

Page _____

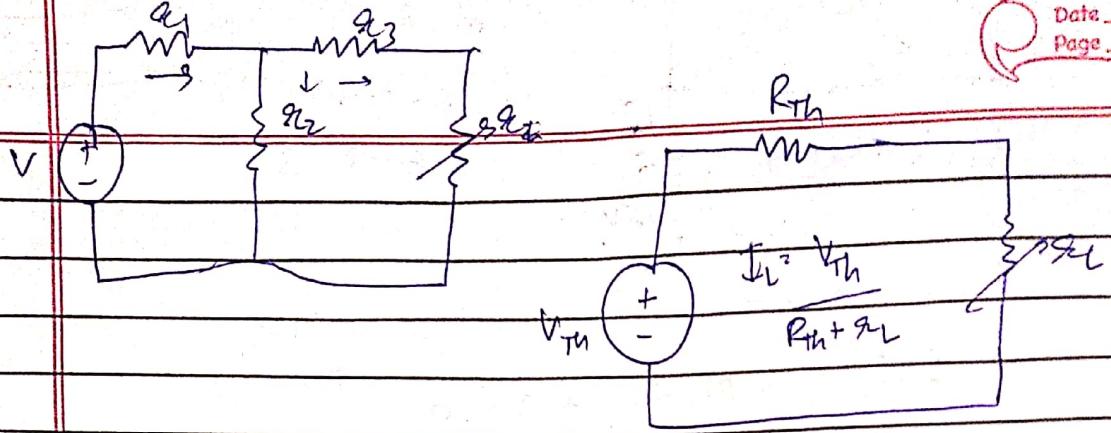


- ① Remove load resistor and find V_{oc} → open circuit voltage across load resistor.

- ② ~~Voltage~~ Replace independent sources with their internal resistance


voltage dependent $\rightarrow k_1 R_1 = 0 \rightarrow$ close circuit \rightarrow short circuit






current dependent \rightarrow infinite \rightarrow open circuit.

- ③ Draw thevenin equivalent circuit




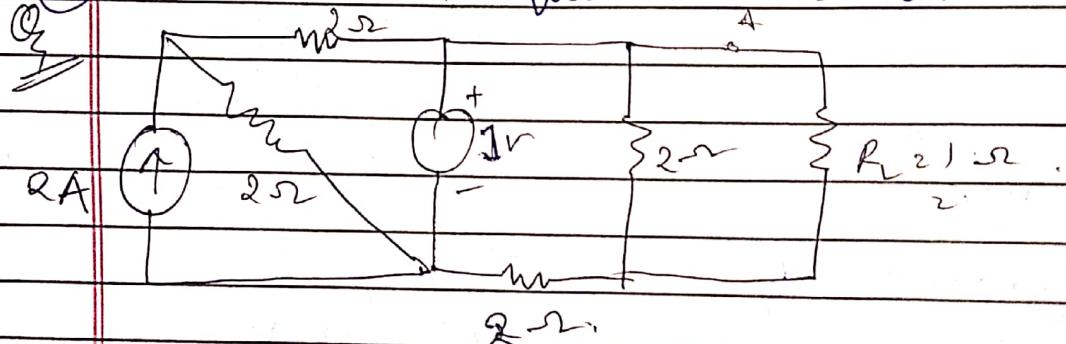


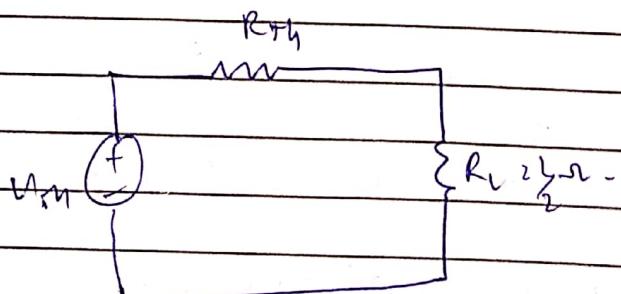find V_{th} and R_{th} across terminals A & B.




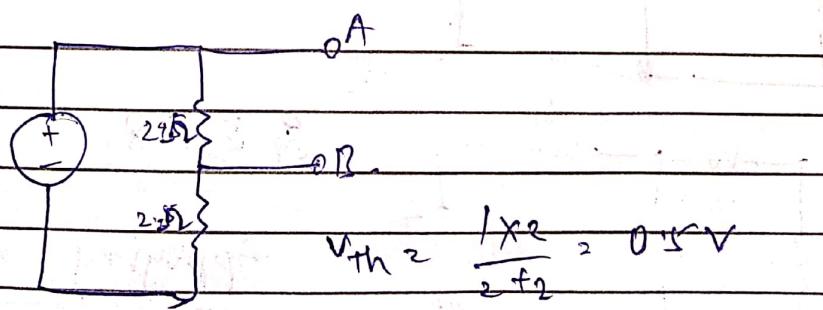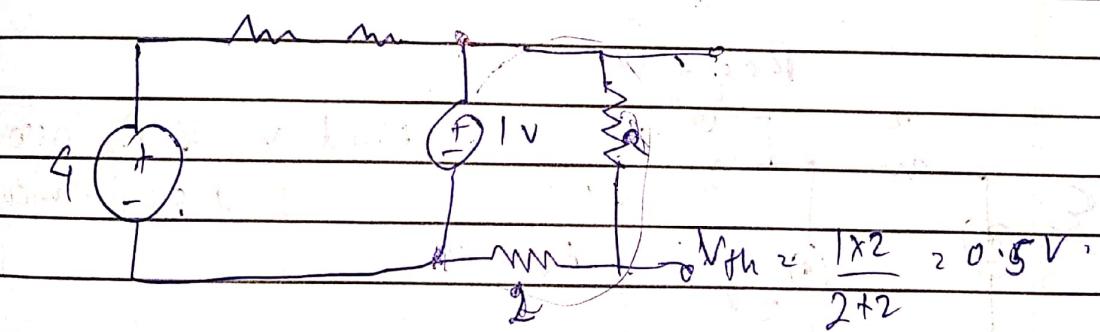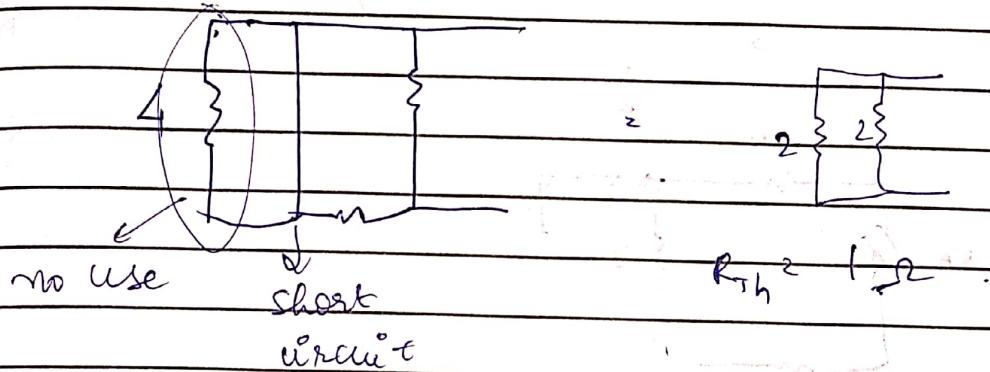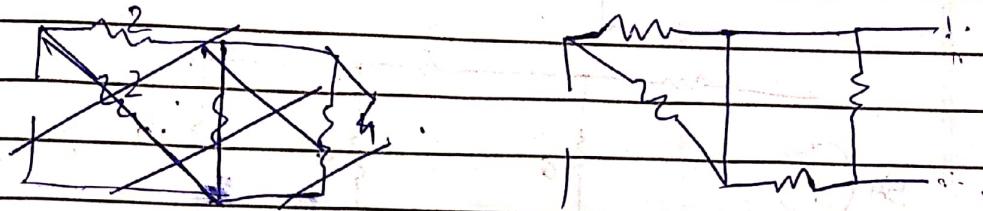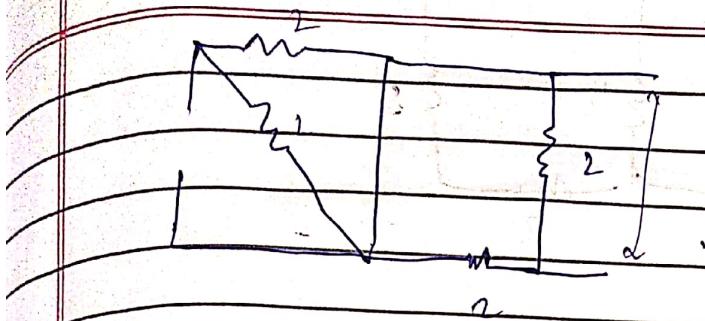
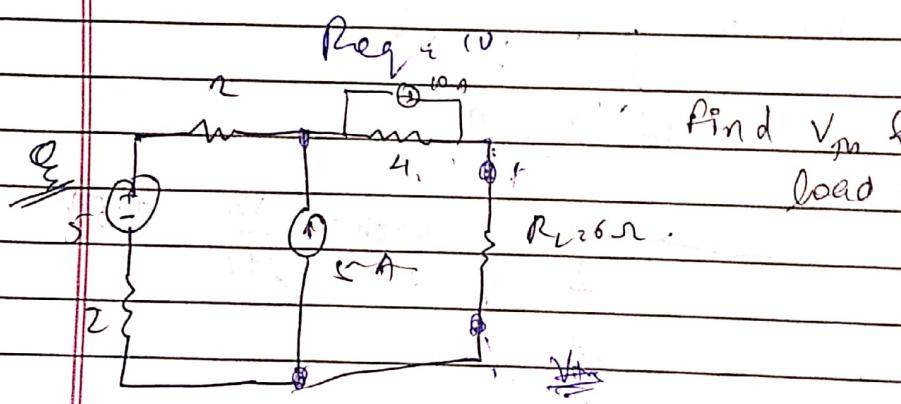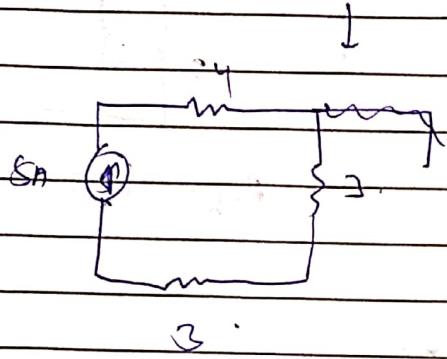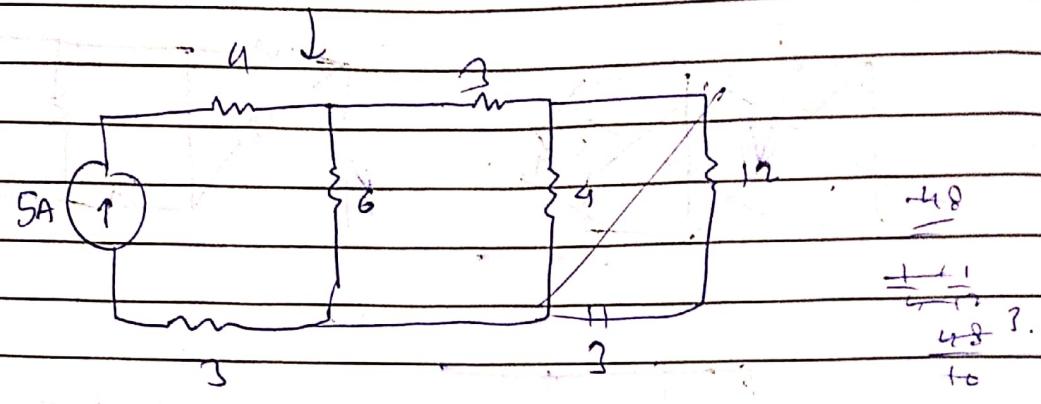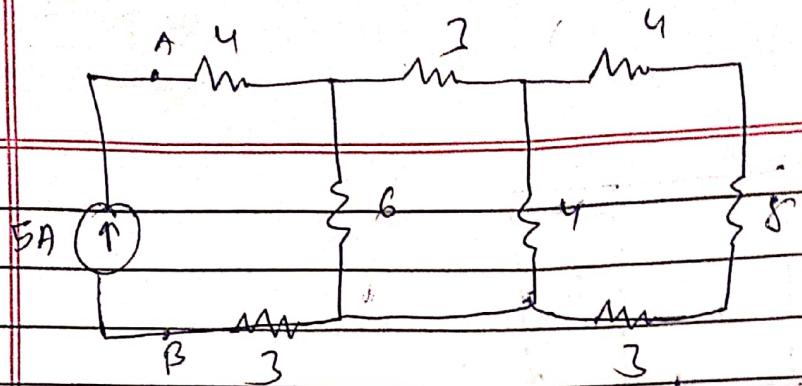
$$\frac{V_{th}}{R_{th} + R_2} = \frac{0.5}{1 + 0.5} = \frac{1}{3}$$




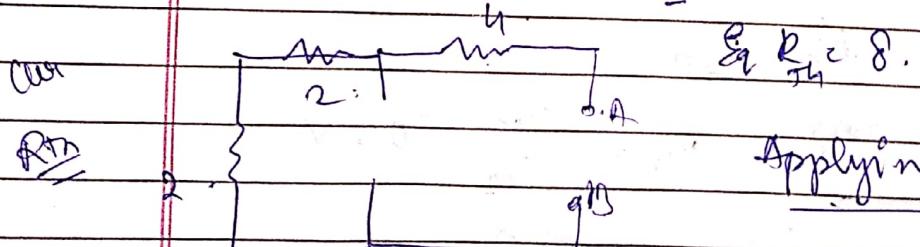Req ≈ 10 .
Find V_m & R_m across
load resistance.



$\therefore R_m \approx 8$.
Applying nodal

2

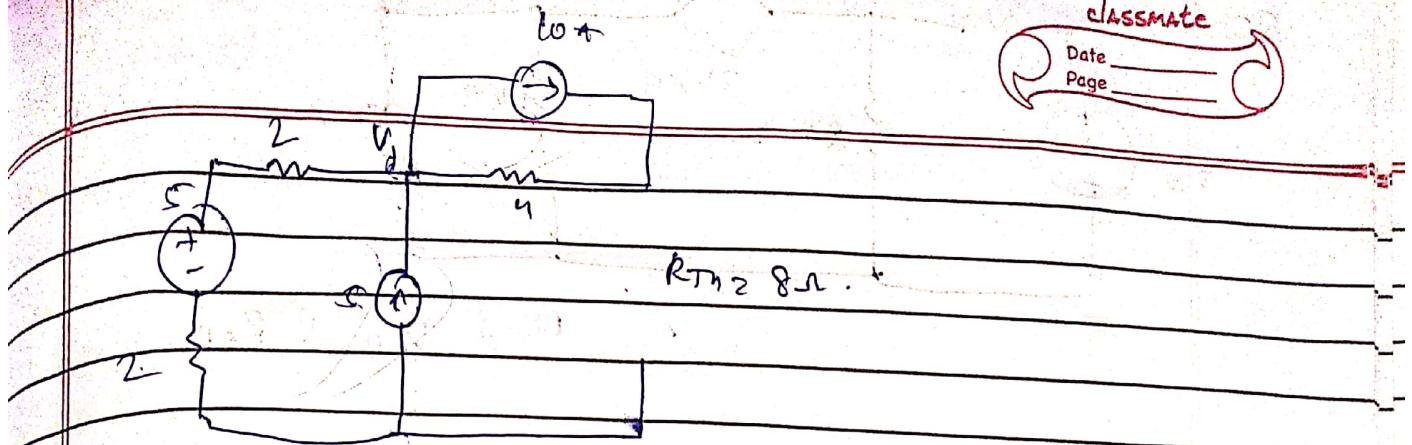



$$\frac{V_1 - 5}{4} - 5 + \frac{V_1 - V_{Th}}{4} + 10 = 0.$$

$$\frac{V_{Th} - V_1}{4} - 10 = 0.$$

$$V_1 = 25^\circ$$

$$\frac{V_{Th} - 25}{4} = 10 \rightarrow 0$$


$$V_{Th} = 65^\circ$$

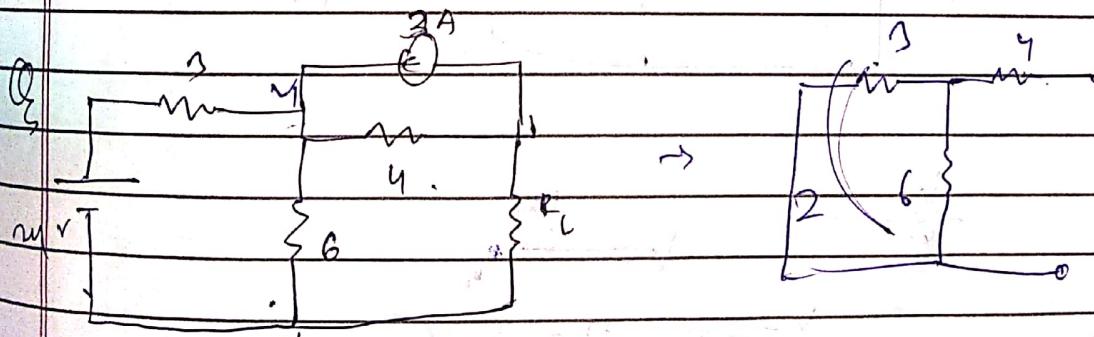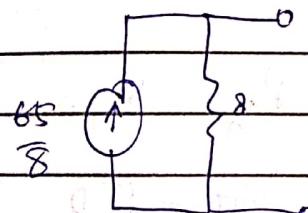

$$\frac{2 \times 6}{9} = 2.$$



$$\frac{V_1 - 24}{3} + \frac{V_1 - 3}{4} + \frac{V_1 - V_{Th}}{6} + V_1 = 0 \therefore R_{Th} = 6.$$
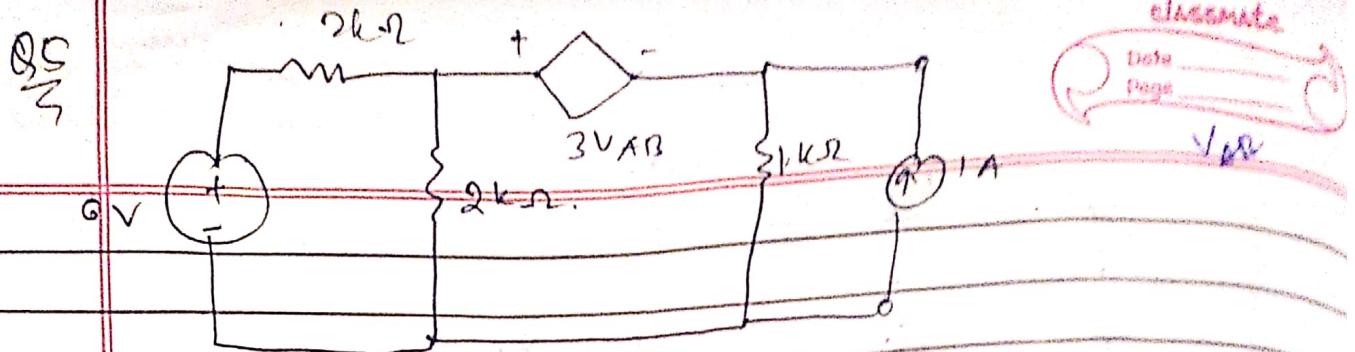
$$\frac{V_{Th} - V_1 + 3}{1} = 0 \quad \frac{V_{Th} - 16 + 3}{6} = 0; \quad V_1 = 16 \rightarrow V_{Th} = 4.$$



Find V_{AB} & P_{AB} .

Q

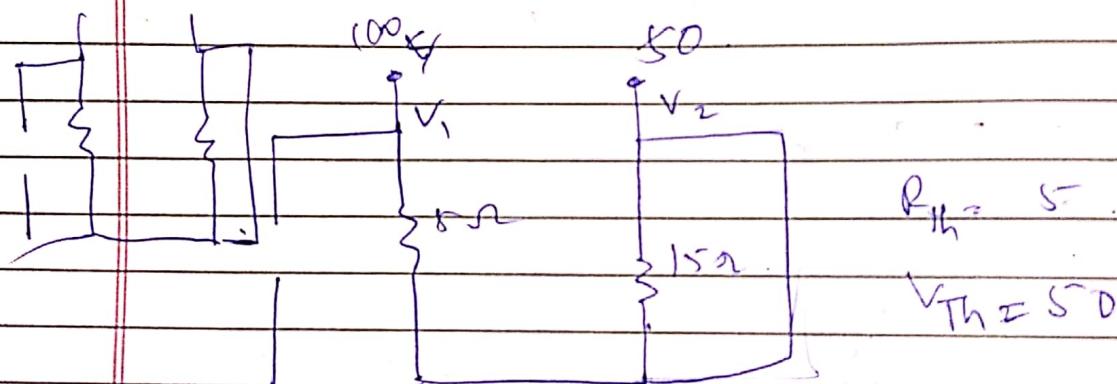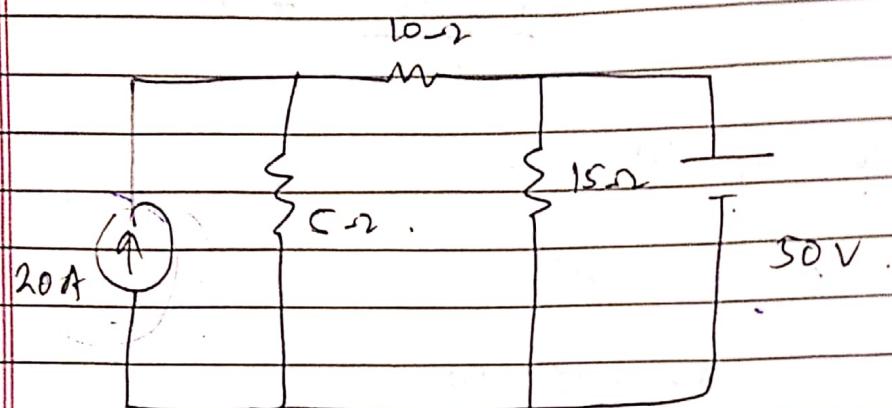

$$V = 20 - 20 + V$$

$$\frac{V}{5} + \frac{V - 50}{15} = 0$$

$$V_o = 20 + V_{-} - 20 = V_{-}$$

$$-8 \quad 15,$$

$$V_{-} = V_{-} - 50 = 20$$



$$-8 \quad 15$$

$$V_o = V_{-} - 50 = 20$$

$$-15$$

$$V_o = 20 - 50 = -30$$

$$V_{TH} = 50$$

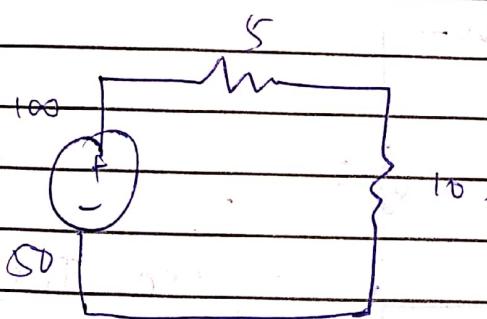
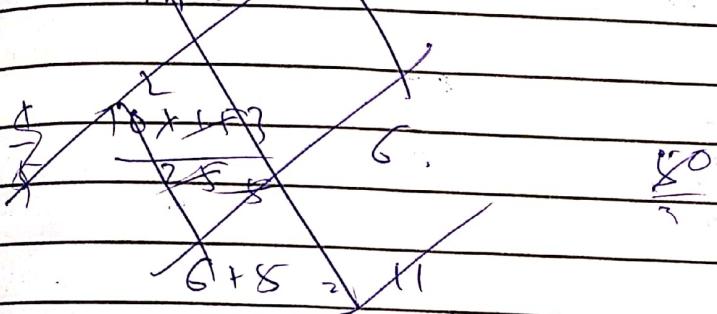


$$I_L = \frac{50}{5+10} = 3.33A$$

NORTON'S THEOREM


classmate

Date _____
Page _____

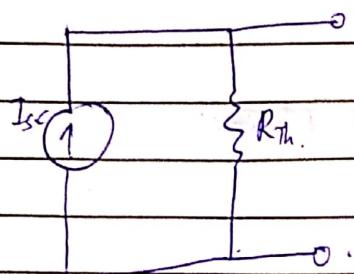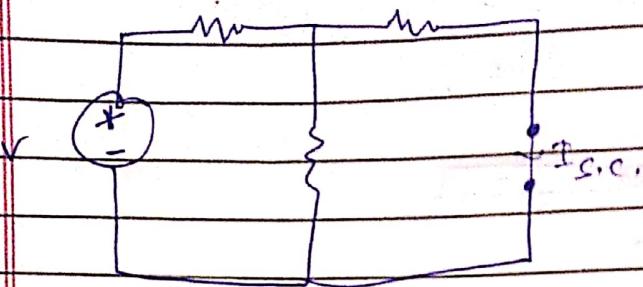


$$I_1 = \frac{V}{R_1 + R_2 R_3}$$

$$\frac{R_2}{R_2 + R_3}$$



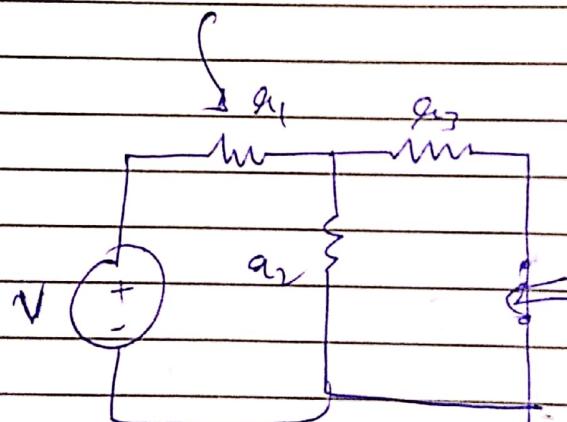


$$I_{S.C.} = I_1 \times \frac{R_2}{R_2 + R_3}$$
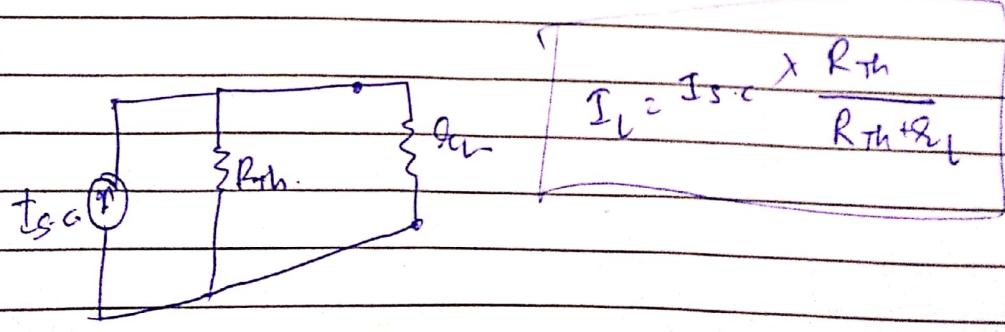
$$R_{Th} = R_3 + \frac{R_1 R_2}{R_1 + R_2}$$


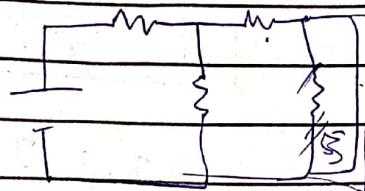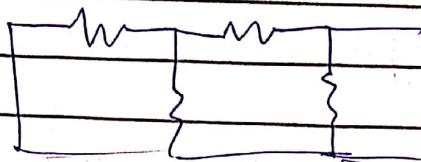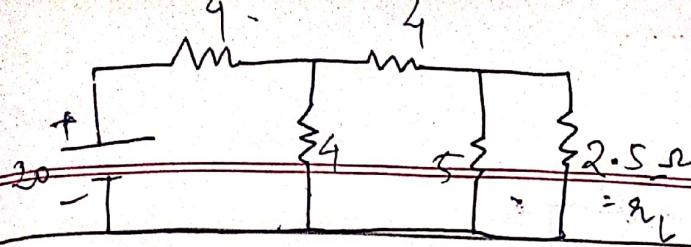
$$I_L = I_{S.C.} \times \frac{R_{Th}}{R_{Th} + R_L}$$



$$2 + 4 = 6.$$

$$\frac{20}{9} + \frac{16}{8}$$

2 eq resist
+ance.

~~Excess~~

~~20~~
~~4~~

$$I_{SC} = \frac{3.3 \times 4}{4 + 4} = 1.66.$$

~~2x1~~
~~2x1~~
~~2x1~~



$$I_C = 1.66 \times \frac{30}{11}$$

$$0.86 A.$$

$$2.5 + 30$$

$$= \frac{30}{11}$$

$$R_{ph} = \frac{30}{11}$$

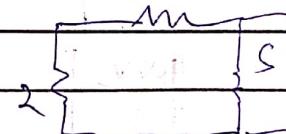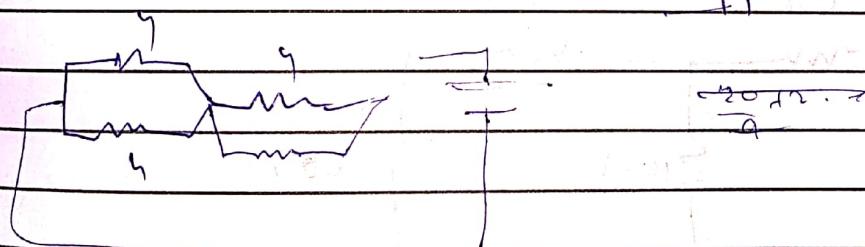


Opamp biasing with 10V

2.5V

2.5V

2.5V

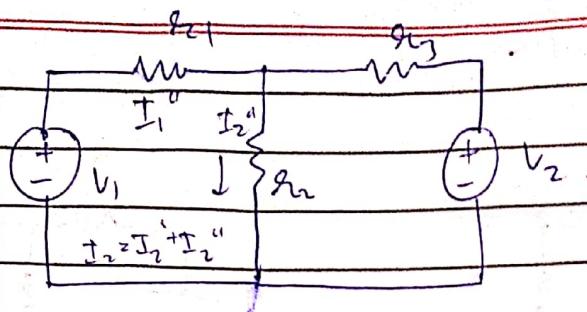Superposition

$$I_1 = I_1' - I_1''$$

$$I_3' = I_1' \times \frac{R_2}{R_2 + R_3}$$


$$I_3 = I_3' - I_3''$$

$$I_2' = I_1' - I_1''$$


$$I_3'' = \frac{V_2}{R_3 + \frac{R_1 R_2}{R_1 + R_2}}$$

$$I_1'' = I_2'' \times \frac{R_1}{R_1 + R_2}$$

$$I_2'' = I_2' - I_1''$$

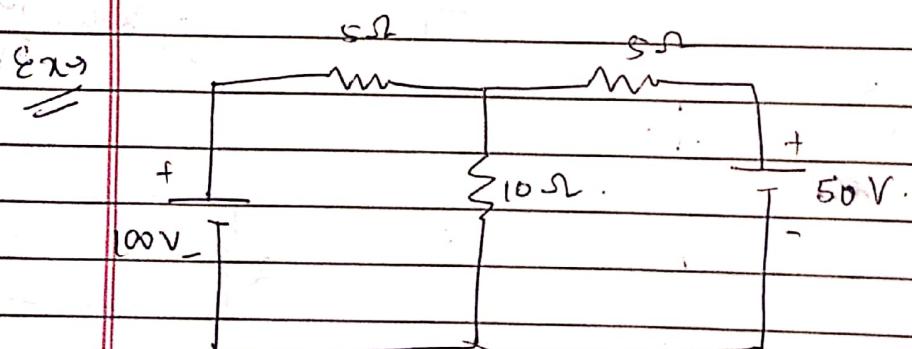

short circuiting one source

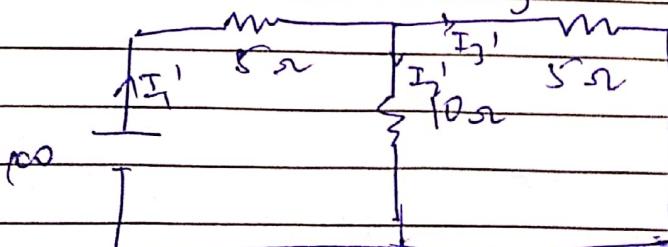

$$\frac{10}{2} + 5 = \frac{25}{2}$$


$$\frac{10 \times 5}{15} = \frac{50}{15}$$

$$I_2 = I = \frac{100}{\frac{20}{3}} = 4A$$

$$I_2' = \frac{5 \times 12}{15} = 4A$$

$$I_3' = 8A$$

Now short circuit other source.

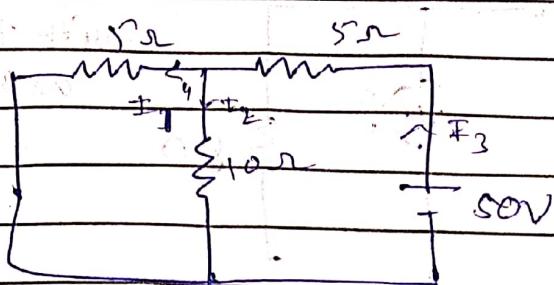

$$\text{Eq. resistance} = \frac{50}{\frac{20}{3}} = 6\Omega$$


$$\frac{20}{3}$$

$$I_1' = \frac{100 \times 3}{20} = 15A$$

$$I_2' = \frac{50 \times 3}{15} = 10A$$

$$I_3' = 6A$$



$$I_1' = 15A$$

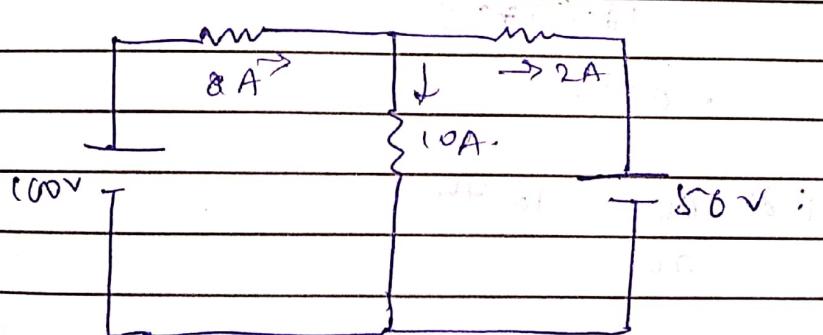

$$I_1 = 8A$$

$$I_2 = 6A$$

$$I_3 = 2A$$

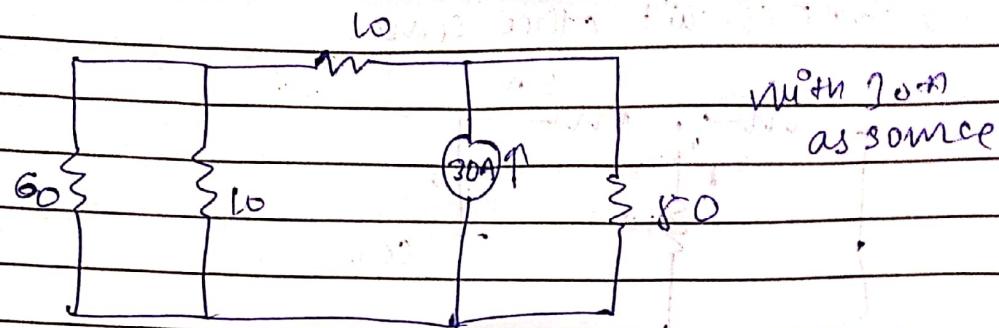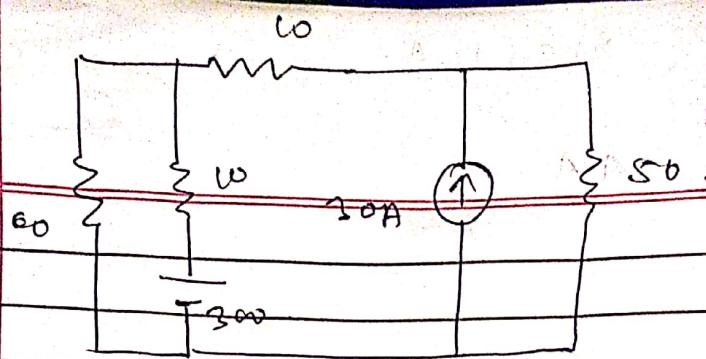

$$60 \parallel 10$$

$$\frac{60 \times 10}{60 + 10} = \frac{60}{7}$$

$$120 \parallel 50$$

60 series 10

$$\frac{60 + 10}{7} = \frac{130}{7} = 18.57$$


$$30 \times 18.57$$

$$18.57 + 50$$

$$= 81$$


$$21.87 \times 60 = 18.74$$

$$70$$

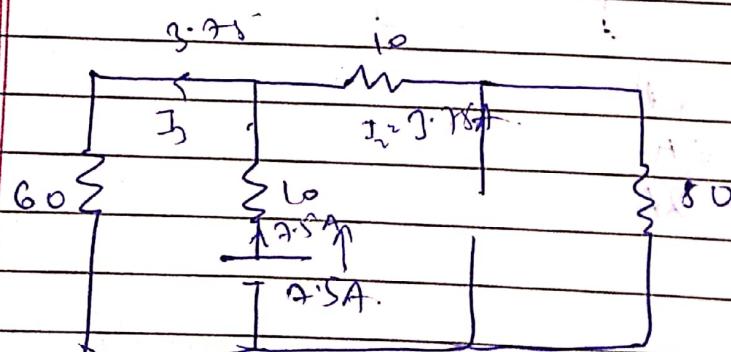

$$I_1 = \frac{300}{10 + \frac{60 \times 60}{60 + 60}} = 7.5 \text{ A}$$

Total equivalent

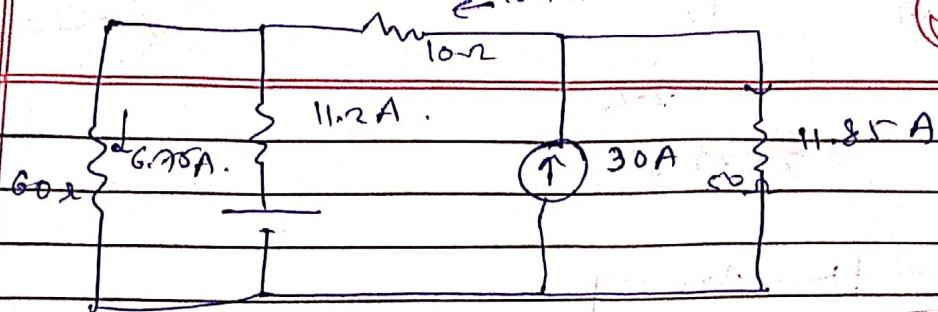


classmate

Date _____

Page _____

MAXIMUM POWER EQUIVALENT THEOREM


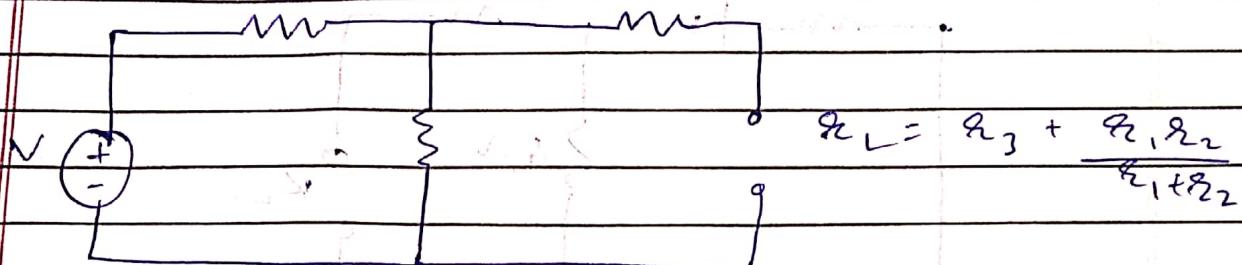


$$P = I_L^2 R_L$$

$$P = \left(\frac{V_{th}}{R_{th} + R_L} \right)^2 \times R_L$$

$$R_{th} = R_L$$

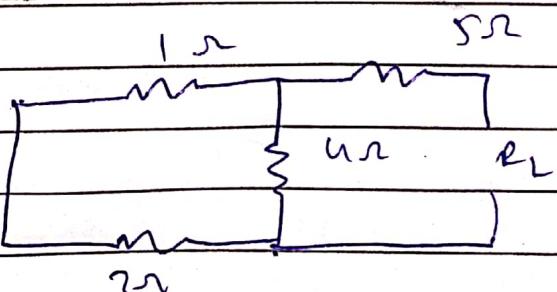
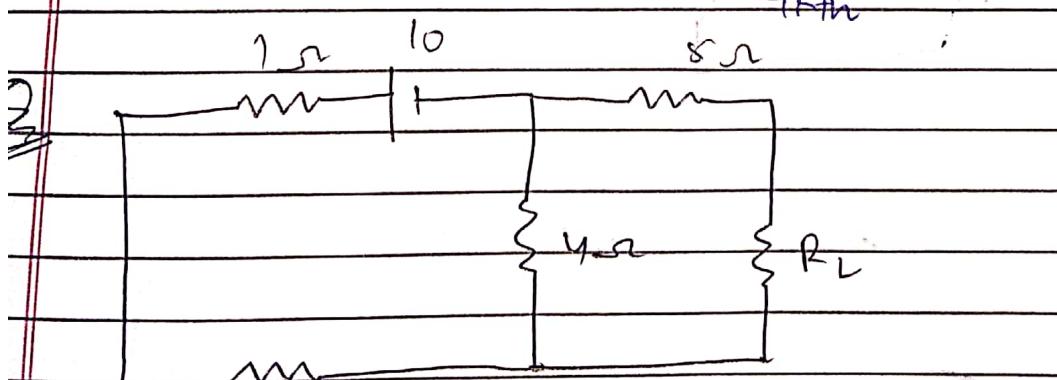
$$P_{max} = \frac{V_{th}^2}{4R_{th}}$$
 for maximum power.



$$R_L = 7\Omega$$

$$\frac{u}{u+u+12} \times 10 = \frac{u}{16} \times 10$$

$$2.5 \\ = 2.5 \times 2.5 = 6.25$$

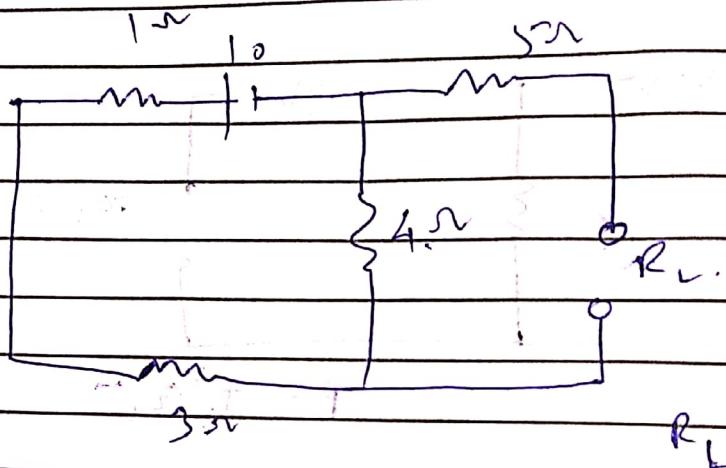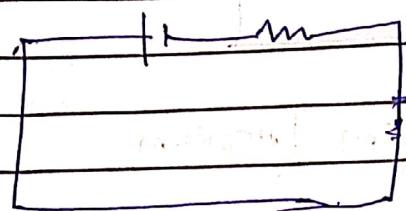

$$R_L = 7$$

$$10/2 = 1.25$$

$$R_{th} = 7$$

