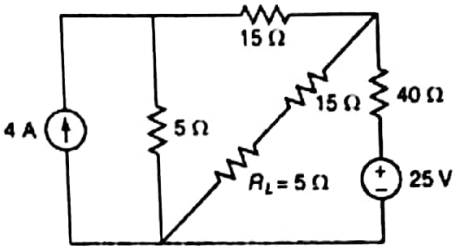
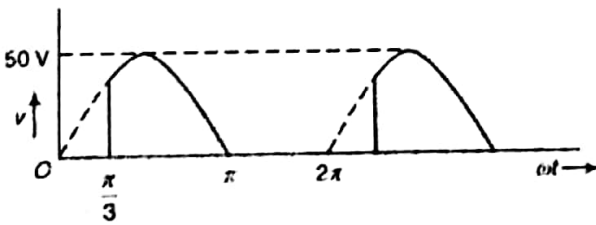


NOTE: All questions carry equal marks. **FULL CREDIT** is due only to legible, systematically written to the point correct answers.

Q.1	<p>Using the superposition theorem, find the current through <math>R_L</math> in the circuit shown in figure.</p> 
Q.2	<p>A circuit takes a current <math>i = 50 \sin(314t - \pi/3)</math> when the supply voltage is <math>v = 400 \sin 314t</math>. Find the impedance, resistance, and the inductance of the circuit.</p>
Q. 3	<p>The resistor and a capacitor are connected in series with a variable inductor. When a circuit is connected to a 240 V, 50 Hz supply, the maximum current by varying the inductance is 0.5 A. At this current the voltage across the capacitor is 250 V. Calculate R, C and L</p>
Q. 4	<p>Find the average and rms value of the waveform shown in Figure.</p> 

Subject Coordinator: Dr S C Gupta