

Name of student \_\_\_\_\_

Roll No \_\_\_\_\_

**MAULANA AZAD NATIONAL INSTITUTE OF TECHNOLOGY**  
**DEPARTMENT OF ELECTRICAL ENGINEERING**  
**Mid Term Examination March 2024**  
**B. Tech I Semester (E- Section)**

Subject: Basic Electrical &amp; Electronics Engg (EE108)

Date of Exam-21/03/2024

Time: 90 Minutes [9:30-11:00 AM]

Max. Marks: 20

NOTE: All question carry equal marks. FULL CREDIT is due only to legible, systematically written to the point correct answers.

Q.1	Find $I_1$ , $I_2$ and $I_3$ in the network, using loop-current method.
Q.2	Why average power consumed in pure capacitive circuit is zero? . How does capacitive reactance vary with frequency?
Q.3	<p>A coil of inductance 0.64 H and resistance 40 <math>\Omega</math> is connected in series with capacitor of capacitance 12 <math>\mu</math>F.</p> <p>Estimate :</p> <p>(i) The frequency at which resonance will occur.</p> <p>(ii) The voltage across the coil and capacitor, respectively and also the supply voltage when a current of 1.5 A at the resonant frequency is flowing.</p> <p>(iii) The supply voltage with a current of 1.5 A flowing at a frequency of 50 Hz.</p>
Q.4	<p>Perform the open circuit test on 230/115 V 15 kVA transformer and answer the following in brief-</p> <p>(i) What is the purpose of this test?</p> <p>(ii) Why the power factor becomes low during the test?</p> <p>(iii) How much voltage you need to apply &amp; why?</p> <p>(iv) What will happen if you apply only 100 V to perform this test?</p>
Q.5	<p>A 230 V/115 V single-phase transformer takes a no-load current of 2 A at a power factor of 0.2 lagging with low voltage winding kept open. If the low voltage winding is now loaded to take a current of 15 A at 0.8 power factor lagging find the current taken by high voltage winding. Draw the vector diagram showing all angles and no load current.</p>