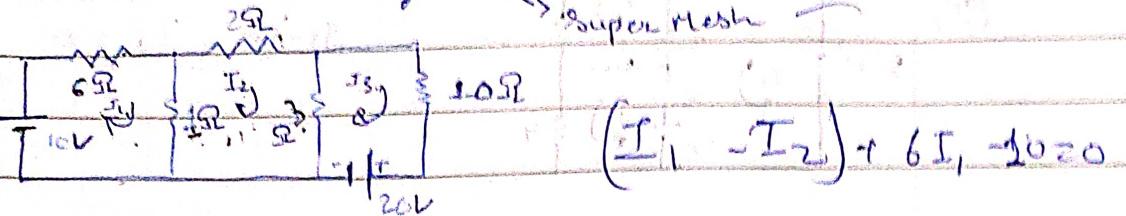


Mesh Analysis  $\rightarrow$  Normal Mesh  $\rightarrow$  Mesh with current source  $\rightarrow$  Super Mesh

Q1)



$$(I_1 - I_2) + 6I_1 - 10 = 0$$

Applying KVL in mesh 1:

$$1(I_1 - I_2) + 6I_1 - 10 \Rightarrow 7I_1 - I_2 = 10 \quad (1)$$

$$3(I_2 - I_3) + 1(I_2 - I_1) + 2I_2 = 0 \Rightarrow -I_1 + 6I_2 - 3I_3 = 0$$


$$10I_3 + 3(I_3 - I_2) + 20 = 0 \Rightarrow 13I_3 - 3I_2 = -20$$

$$I_3 = 1.68$$

$$I_1 = 1.34$$

$$I_2 = -0.61$$

Q2)

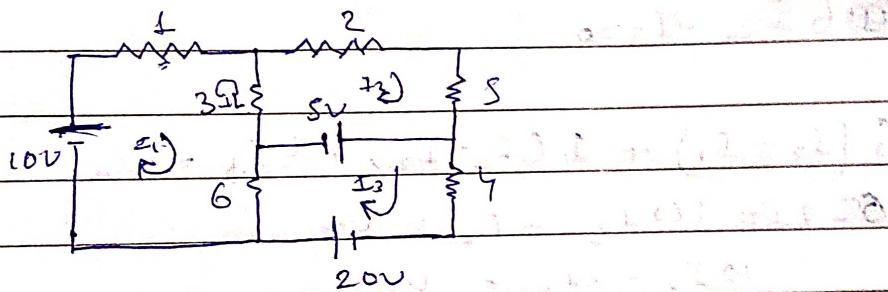

$$I_1 + 3I_1 + 6I_1 + 3(I_1 - I_2) + 6(I_1 + I_3) = 10$$

$$10I_1 - 3I_2 - 6I_2 = 10$$

$$2I_2 + 5I_2 + 3(I_2 - I_1) = 5$$

$$-3I_1 + 10I_2 = -5$$


$$4I_3 + 6(I_3 - I_1) = 25$$

$$10I_3 - 6I_1 = 25$$

$$I_1 = 4.274$$

$$I_2 = 0.784 A$$

$$I_3 = 5.06 A$$

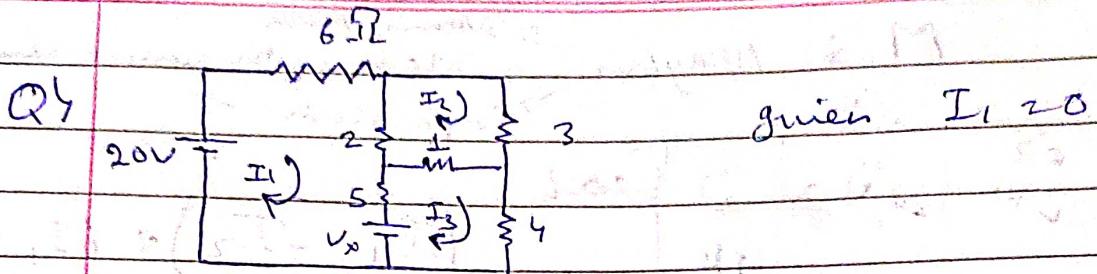

$$2(I_1 - I_2) + 5(I_1 - I_3) + 6I_1 = -V_x + 20$$

$$2I_1 - 2I_2 + 5I_1 - 5I_2 + 6I_1 = -V_x + 20$$

~~$$13I_1 - 7I_2 - 5I_3 = -V_x + 20$$~~

~~$$2I_2 - 5I_3 + V_x = 20 \quad (1)$$~~

$$3I_2 + I_2 - I_3 + 2I_2 - 2I_2 = 0$$

~~$$6I_2 - I_3 = 0$$~~

$$5(I_3 - I_1) + 1(I_3 - I_2) + 4I_3 = V_x$$


~~$$6I_3 + 10I_3 - I_2 = V_x$$~~

$$10I_3 - 2I_2 = -V_x = 20$$

$$I_3 = 4.4 \text{ mA}$$

$$I_2 = 0.7 \text{ mA}$$

$$V_x = 43.7 \text{ V}$$

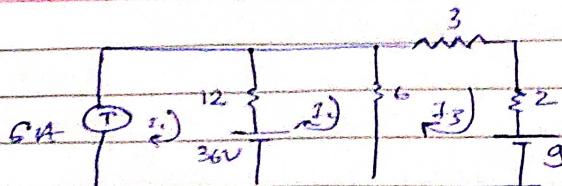

$$I_1 = 6 \quad \text{①}$$

mesh 2 KVL

$$6 I_2 - 6 I_3 + 12 I_2 - 12 I_1 = 36$$


$$18 I_2 - 6 I_3 = 36 \quad 108 \quad \text{②}$$

Mesh 3 KVL

$$3 I_3 + 2 I_3 + 6 I_3 - 6 I_2 = -9$$

$$11 I_3 - 6 I_2 = -9 \quad \text{③}$$

$$I_2 = 7A, I_3 = 3A \quad (\text{④})$$

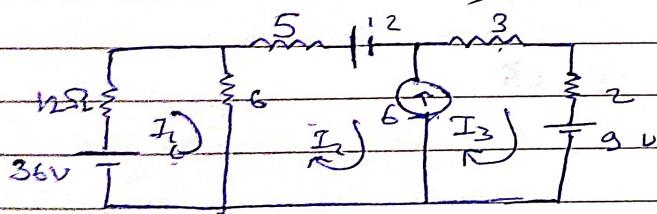

① → current source

$$36 = 18 I_1 + 6 I_2 \quad \text{⑤}$$

$$12 I_1 + 6 I_1 - 6 I_2 = 36$$

$$18 I_1 - 6 I_2 = 36 \quad \text{⑥}$$

writing current for supermesh


$$I_3 - I_2 = 6$$

Mesh 2 and 3 form supermesh

$$6(I_2 - I_3) + 5I_2 + 3I_3 \quad \text{⑦} \quad 72I_3 = -21$$

$$6I_2 - 6I_3 + 5I_2 + 3I_3 + 2I_3 = -21$$

Q4

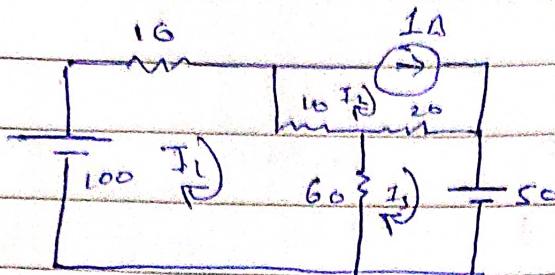

$$I_2 = 1 \quad (1)$$

KVL to Mesh 1

$$10(I_1 - I_2) + 60(I_1 - I_3) + 10I_2 = 100 \quad (1)$$

$$80I_1 - 10I_2 - 60I_3 = 100 \quad (2)$$

$$-80I_2 - 60I_3 = 100 \quad (3)$$

KVL to Mesh 3

$$60(I_3 - I_1) + 20(I_3 - I_2) = -50$$

$$-60I_1 - 20I_2 + 80I_3 = -50 \quad (4)$$

$$-60I_1 + 80I_3 = -30 \quad (5)$$

Ans

V<sub>A</sub> kitaraf + hai to -

PAGE NO.:  
DATE: / /

## Nodal Analysis $\xrightarrow{\text{Normal current source}}$ $\xrightarrow{\text{super node}}$


Steps:

→ Identify nodes

→ II equipotential node  $\rightarrow$

II ground node

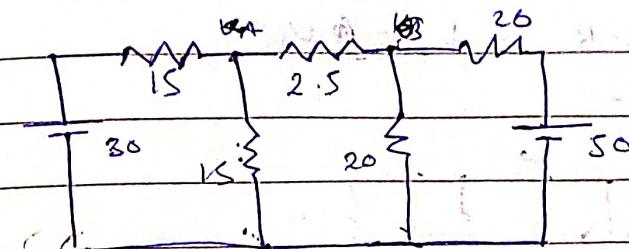→ Apply formula and solve  $\rightarrow$  Formula  $\Rightarrow$  jaisa ek  
formula wa-  
saha p. e.




Formula:

Jaha se nikal raha hai?

- Jaha pe jo raha hai  $+/- V$

Resistance

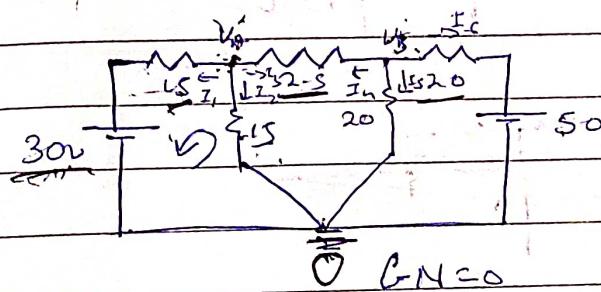

DRR

Applying KCL to V<sub>A</sub>

$$I = \frac{V}{R}$$

$$\frac{V_A - (-30)}{15} + \frac{V_A}{15} + \frac{V_A - V_B}{2.5} = 0 \quad \text{①}$$

$$\frac{V}{R} = I$$

$$8V_A - 6V_B = 30 \quad \text{②}$$


$$\frac{V_B - 50}{20} + \frac{V_B}{20} + \frac{V_B - V_A}{2.5} = 0 \quad \text{③}$$

$$\frac{8V_B - 8V_A + V_B + V_B - 50}{20} = 0$$

$$-8V_A + 10V_B = 50 \quad \text{④}$$

$$V_A = 18.75 \quad , \quad V_B = 20$$




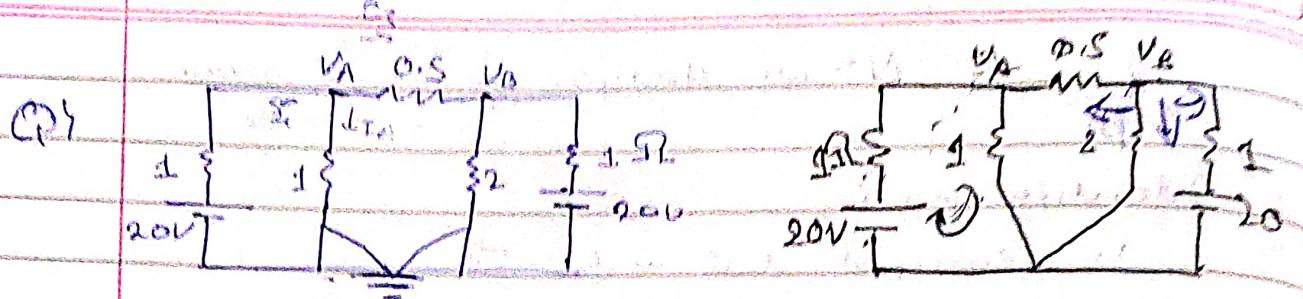
$$\frac{V_A - V_B}{2.5} = \frac{18.75 - 20}{2.5} = -0.5A$$



$$\frac{V_A - 20}{1} + \frac{V_A - V_n}{1} + \frac{V_n - V_B}{0.5} = 0$$


$$\frac{V_B - 20}{1} + \frac{V_B - V_A}{1} + \frac{V_A - 10}{0.5} = 0$$

(Q2)

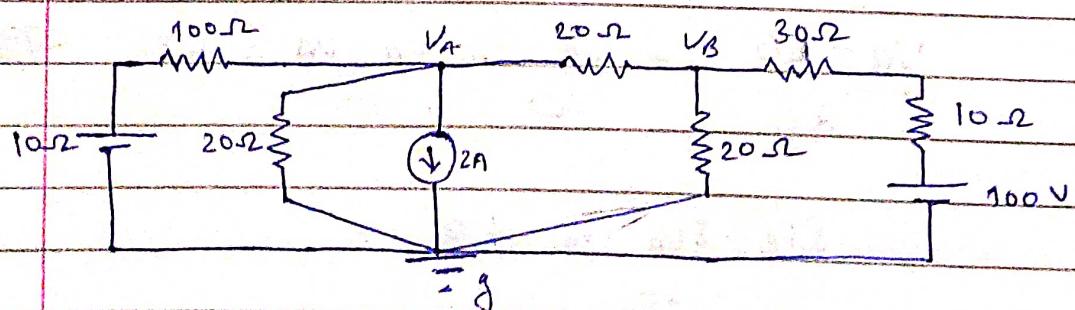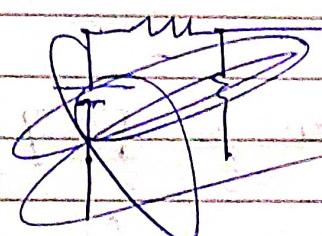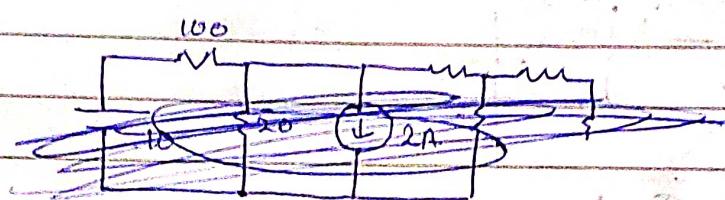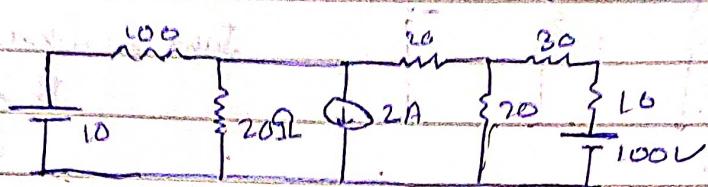

$$\frac{V_A - 10}{100} + \frac{V_A - V_B}{20} + 2 = 0$$
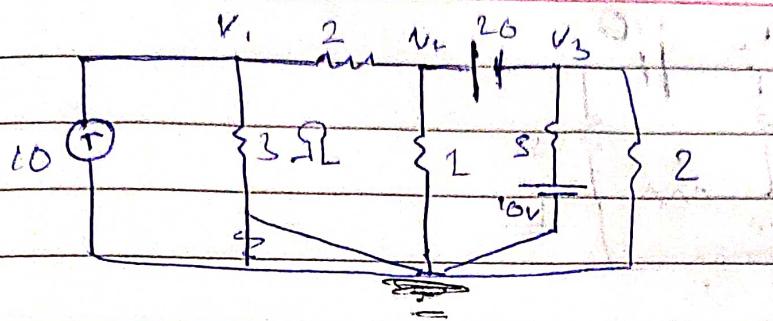
$$\frac{V_B}{20} + \frac{V_B - V_A}{20} + \frac{V_B - 100}{40} = 0$$




$$-10 + \frac{V_1}{3} + \frac{V_1 - V_2}{2} = 0$$

$$\frac{V_2 - V_1}{2} + \frac{V_2}{1} = 0$$

$$\frac{V_2 - V_3}{2} > 20$$
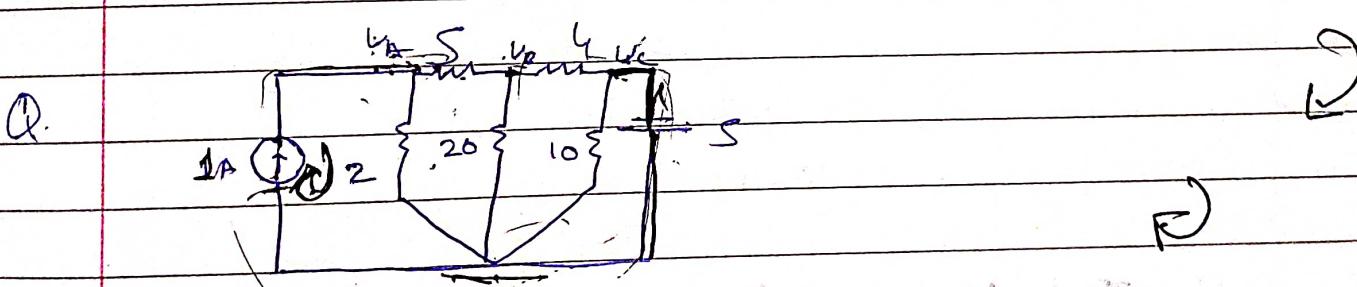
$$\frac{V_2 - V_1}{2} + \frac{V_2}{1} + \frac{V_3}{2} + \frac{V_3 - 10}{5} = 0$$



Applying  $V_A$

$$\frac{V_A}{2} - 1 + \frac{V_A - V_B}{5} = 0$$


Applying  $V_B$

$$\frac{V_B - V_A}{2} + \frac{V_B - V_C}{4} + \frac{V_B}{20} = 0$$

Applying  $V_C$

$$V_C + 5 = 0$$

Q)

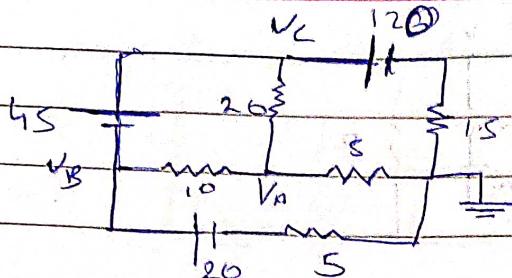

$$\frac{V_A - V_B}{10} + \frac{V_A - V_C}{20} + \frac{V_A}{5} = 0 \quad (1)$$

$$V_B - V_A = 45 \quad (2)$$

$$\frac{V_B - V_A}{10} + \frac{V_B - 20}{5} + \frac{V_C - 120}{15} + \frac{V_C - V_A}{20} = 0$$

$$\frac{V_A}{5} + \frac{V_A - V_B}{10} + \frac{V_A - V_C}{20} = 0$$

$$\frac{V_C - 120}{15} + \frac{V_C - 120}{15} = 0$$

$$\frac{V_B - 20}{5} + \frac{V_B - V_A}{10} = 0$$

$$V_C - V_B = 45$$

# Superposition

PAGE NO.:

DATE: / /


## Basics

1) No of sources + 1 step are used in solving problem


2) Every step should have only 1 source

3) Voltage  $\rightarrow$  short circuit

Current  $\rightarrow$  open

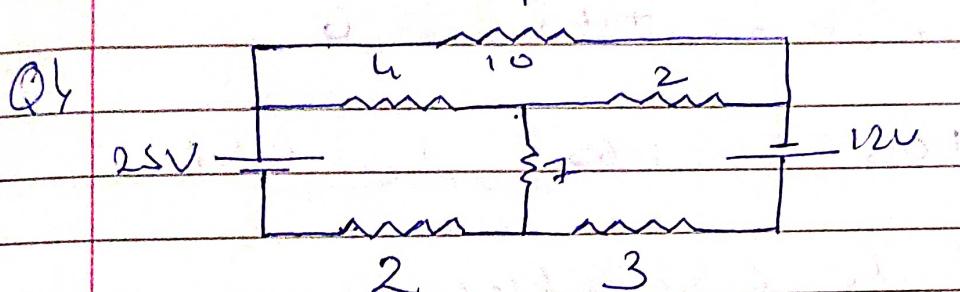

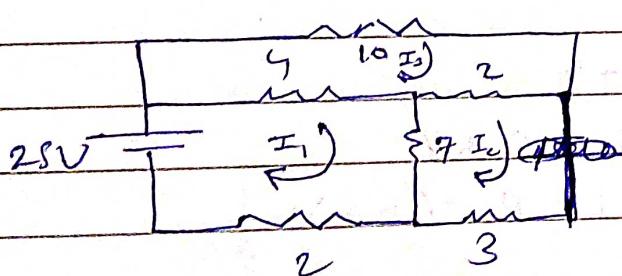Step 1  $\rightarrow$  When 25V is active alone



Applying KVL in Mesh 1

$$13 \times I_1 - 7 I_2 - 4 I_3 = 25$$

Mesh 2

$$-7 I_1 + 12 I_2 - 2 I_3 = 0$$

Mesh 3


$$-4 I_1 - 2 I_2 + 16 I_3 = 0$$

$$I_1 = 3.46 \text{ A}, I_2 = 2.02 \text{ A}, I_3 = 1.14 \text{ A}$$

10Ω के लिए  $I_3$  जारा है

$$I^L = I_3 = 1.14 \text{ A} \quad 10\Omega \rightarrow$$

Step 2

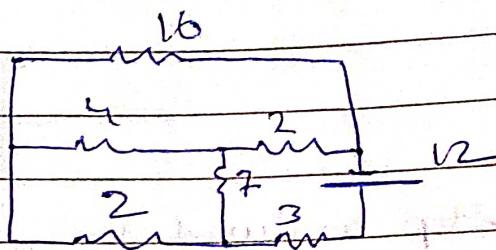

$$+V_3 I_1 - 2 I_2 - 4 I_3 = 0$$

$$-7 I_1 + +V_2 I_2 - 2 I_3 = 12$$

$$-4 I_1 - 2 I_2 + 16 I_3 = 0$$



$$I_1 = 1.06, \quad I_2 = 1.69, \quad I_3 = 0.67$$

$$I^1 = I_3 = 0.67 \text{ A} (\rightarrow)$$

$$\begin{aligned} I &= I^1 + I^2 \\ &= 1.14 + 0.42 \\ &= 1.61 \text{ A} (\rightarrow) \end{aligned}$$

Ans

Q4  
Supermesh

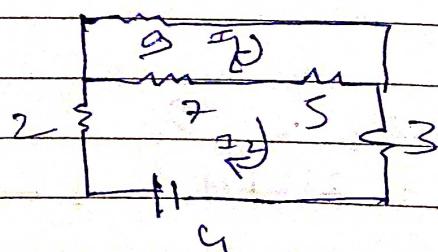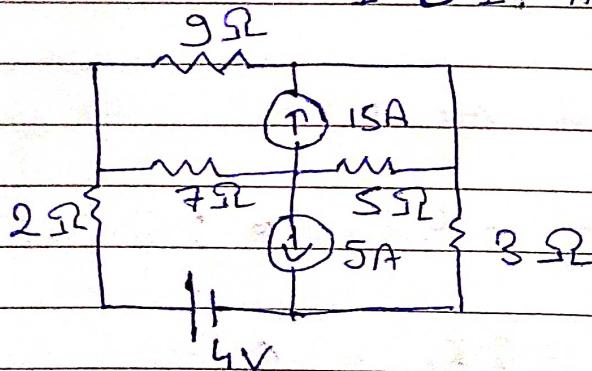


supermesh

$$21 I_1 - 12 I_2 = 0$$

$$-12 I_1 + 17 I_2 = 4$$

$$I_1 = 0.22 \text{ A}, \quad I_2 = 0.39 \text{ A}$$
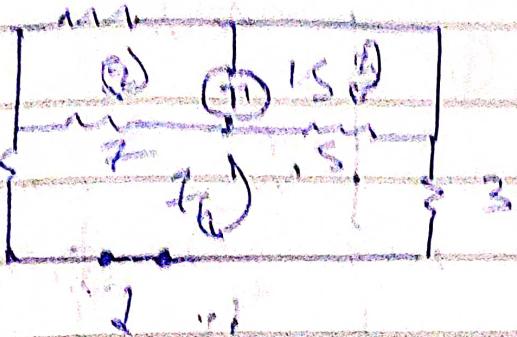
$$I^1 = I_2 = 0.39 \text{ A} (\rightarrow)$$



Short circuit


$$Z \text{ or } 7(I_1 - I_2) + 5(CI_1 - I_3) + 3I_1 + 2I_2 = 0$$

$$7(I_1 - I_2) + 5CI_1 - 5I_3 = 0 \quad (1)$$

$$I_3 - I_2 = 15 \quad (2)$$

$$7(I_2 - I_1) + 9I_2 + 5(I_3 - I_1) = 0$$
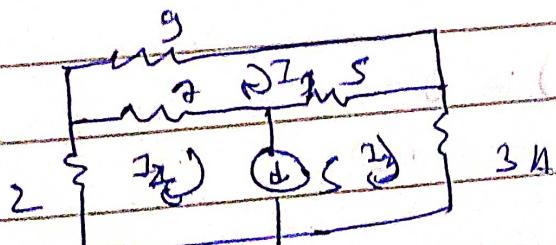
$$I_1 = 3.16 \text{ A}, I_2 = -1.76 \text{ A}, I_3 = 13.23 \text{ A}$$



# Thevenin's Theorem

Steps

Step 1

Calculate  $V_{th}$

By replacing Load Resistance with  $V_{th}$  and  
Solve like Nodal and analysis

Step 2

Calculate  $R_{th}$

Replace

Voltage source  $\Rightarrow$  Short circuit



Current source  $\Rightarrow$  Open circuit


Solve by series parallel method

Step 3

$$\frac{R_{th}}{V_{th}} \quad I_L = \frac{V_{th}}{R_{th} + R_L}$$

Q1

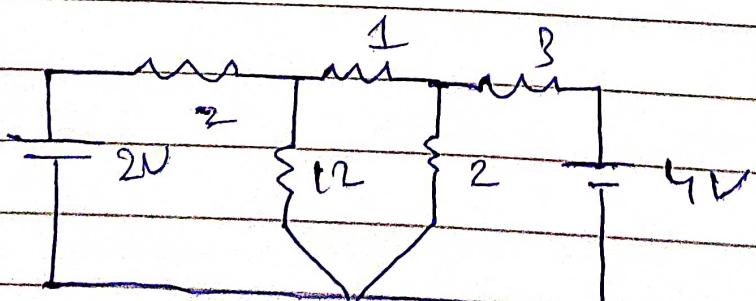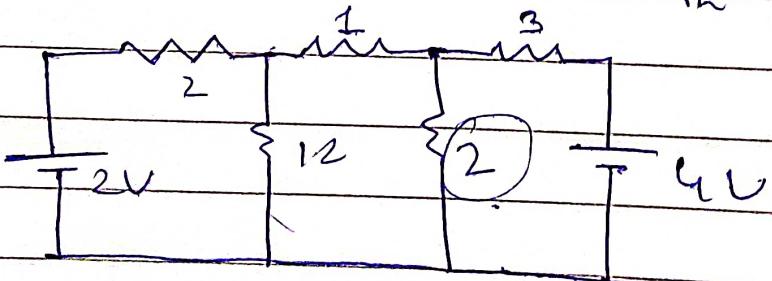

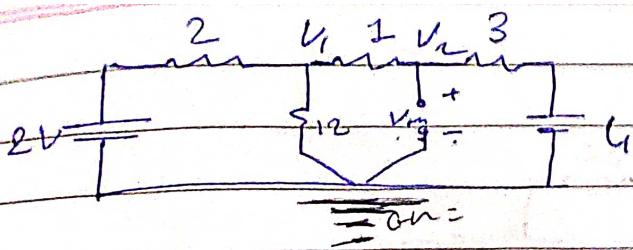

$$\frac{V_1 - 2}{2} + \frac{V_1}{12} + \frac{V_1 - V_2}{1} = 0$$

$$\frac{V_2 - V_1}{1} + \frac{V_2 - 4}{3} = 0$$

$$V_1 = 2.4V \quad V_2 = 2.8V$$

Calculating Voltage  $V_{th}$

$$V_2 = V_{th}$$



$$V_{th} = 2.8V$$

$$\text{As } V_2 - V_{th} - G_n = 0$$


$$V_2 = V_m$$

Calculate  $R_{th}$

$R_{th}$

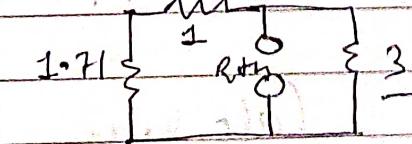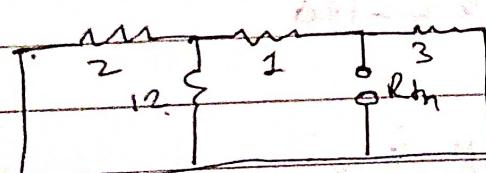

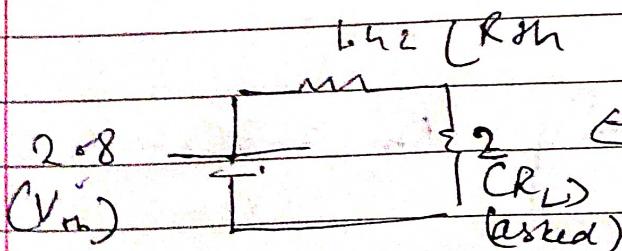as  $2\Omega$  and  $1\Omega$  are parallel  
 $2 \parallel 1 = 1.71$





$$2.71 \parallel 3 = 1.42$$

$$I_L = \frac{2.8}{1.42 + 2}$$

$$V = I_L R_L$$

Q4

$30\Omega$

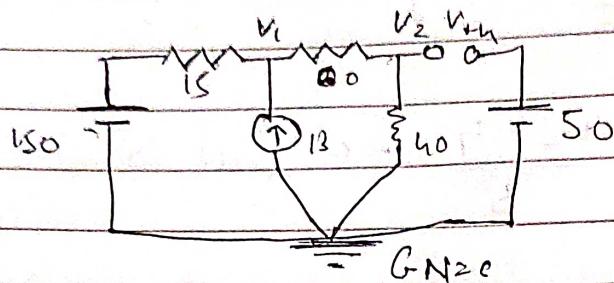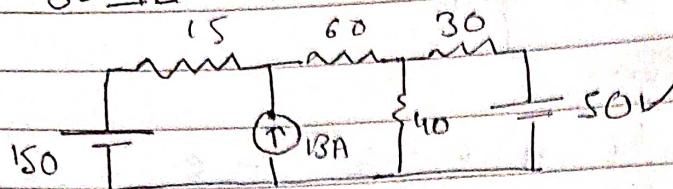

$$\frac{V_1 - 150}{15} + 13 + \frac{V_1 - V_2}{60} = 0$$

$$5V_1 - V_2 = 1380 \quad (1)$$

$$\frac{V_2 - V_1}{60} + \frac{V_2}{40} = 0$$


$$-2V_1 + 5V_2 = 0 \quad (2)$$

$$V_1 = 300, V_2 = 120$$

Calculating Voltage Eqn

$$V_2 - V_{th} - 50 - G_N = 0$$

$$V_{th} = 70V$$

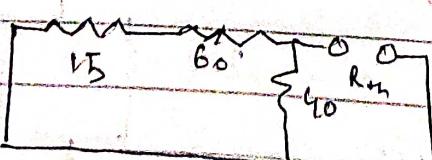

$$R_{th} = \frac{75 \times 40}{75 + 40} = 20\Omega$$


$$I_L = 70 \rightarrow V_{th}$$

$$26.09 + 30$$


through  $R_{th}$

$$\approx 12.6 A$$

(Q3)

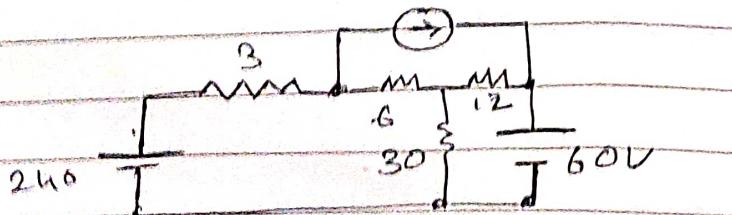

through 12

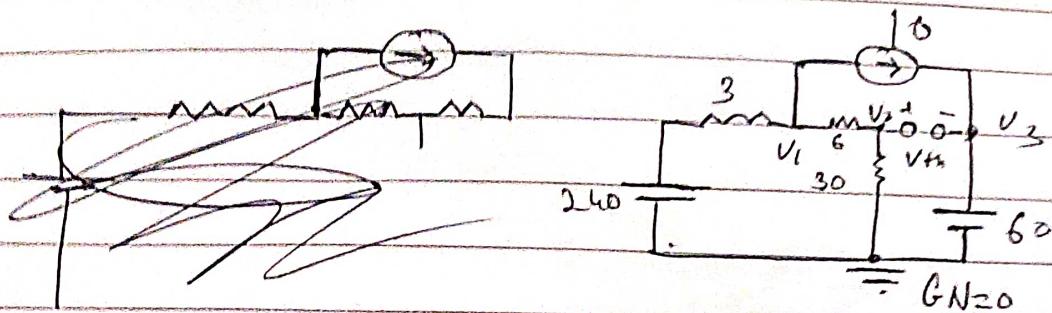

$$\frac{V_1 - 240}{3} + 10 + \frac{V_1 - V_2}{6} = 0$$


$$\frac{V_2 - V_1}{6} + \frac{V_2}{30} = 0$$

$V_3 = 60$  (By observation)

$$V_1 = 193.84 \quad V_2 = 161.53$$

Voltage eq'n  $V_2 - V_m - V_3 = 0$   
 $161.53 - 60 = 0 \quad V_m$

$$V_m = 101.53V$$

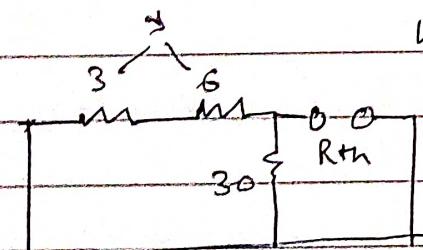


g1130

$$R_m = 6.92$$

$$I_L = \frac{V_m}{R_m + 12} = \frac{101.53}{6.92 + 12}$$

Norton's

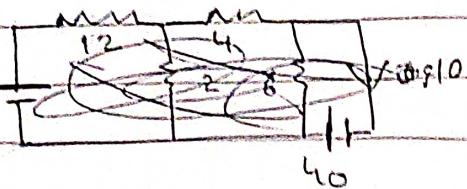

Step 1) Calculate  $I_N$

By replacing load resistance with  $I_N$  and solving like Mesh


Step 2) Find  $R_N$  by replacing voltage  $\xrightarrow{\text{same}}$  short circuit

Current source  $\rightarrow$  open circuit



Step 3) Calculate  $I_L$



$$I_L = I_n R_N / R_N + R_L$$

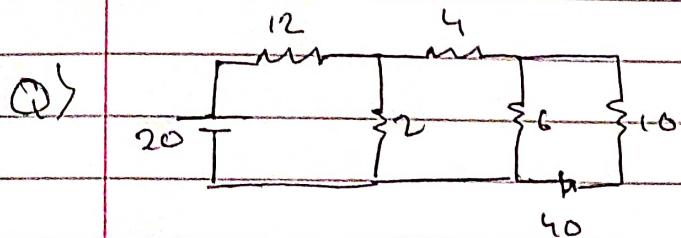

$$\frac{I_n R_L}{R_N + R_L}$$

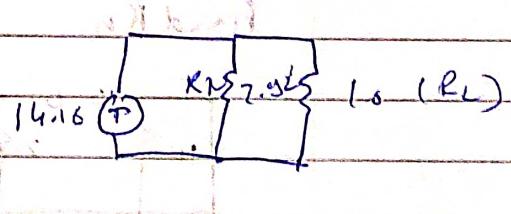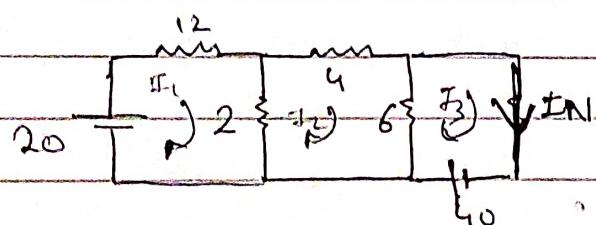

$$14I_1 - 2I_2 - 0I_3 = 20$$

$$-2I_1 + 12I_2 - 6I_3 = 0$$

$$0I_1 + 6I_2 + 6I_3 = 40$$

$$I_1 = 2.5, I_2 = 7.5, I_3 = 14.16$$


$$I_3 = I_n = 14.16A$$

Calculate  $R_N$





$$\frac{I_n R_n}{R_n + R_L}$$
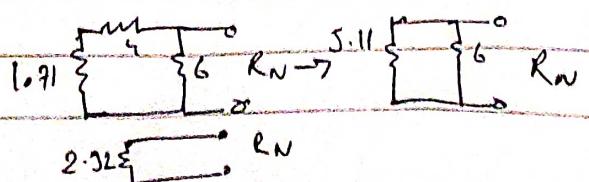
$$\text{Calculate } I_L = \frac{14.16 \times 2.92}{2.92 + 10} = 3.2A$$



Q6

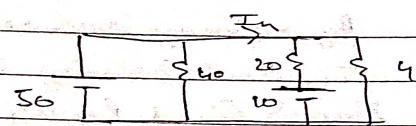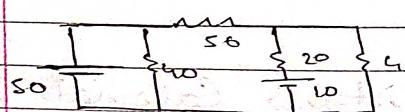

$$40I_1 - 40I_2 - 20I_3 = 50$$

$$-40I_1 + 60I_2 - 20I_3 = -10$$

$$-20I_1 + 20I_2 + 24I_3 = 10$$


$$I_1 = 15.75$$

$$I_2 = 14.5$$


$$I_3 = 12.5$$

$$I_n = I_2 = 14.5$$

Find  $R_n$

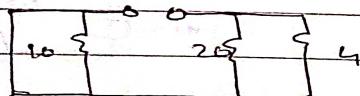
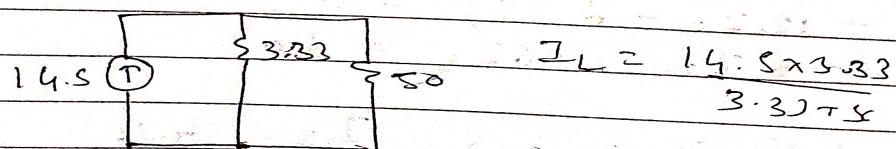
$$\frac{80}{24} \frac{40}{12} \frac{20}{8} \frac{10}{3} \rightarrow 3.33V$$



Step 1

Max power  $\rightarrow$  Calculate  $V_{th}$

by replacing  $R_L$  with  $V_{th}$  with  $\text{No load}$



Step 2  $\rightarrow$  calculate  $R_m$

By replacing Voltage  $\rightarrow$  Short

current  $\rightarrow$  open

Step 3  $\therefore R_L = R_m$

Step 4 : Cal  $P_{max}$

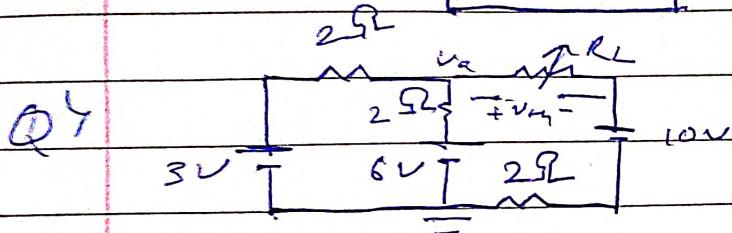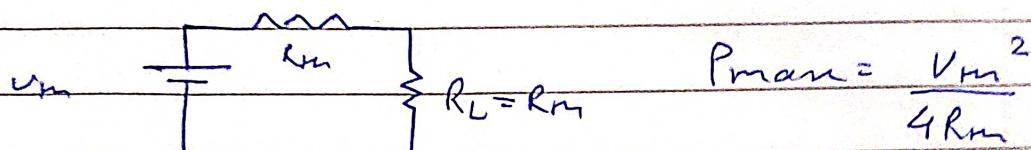


$$\frac{V_A - 3}{2} + \frac{V_A - 6}{2} = 0$$

$$V_A - 9/2 = 0$$

$$V_A - V_m - 10 = 0$$


$\therefore V_m = -5.5$  Do polarity is taken wrong  
(Terminal B is + w.r.t A)

Calculate  $R_m$

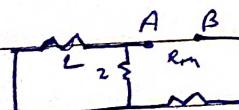

$$R_{AB} = R_m = 3\Omega$$

$$R_L = R_m$$

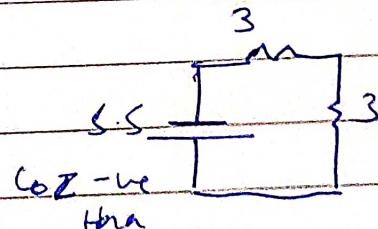

$$P_{max} = \frac{V_{th}^2}{4R_m}$$