

Name of the Student _____

Roll No. _____

MAULANA AZAD NATIONAL INSTITUTE OF TECHNOLOGY

DEPARTMENT OF ELECTRICAL ENGINEERING

Mid Term Exam (May 2023)

Course: **B. Tech**

Subject Name : BEEE

Time : **1 Hours 30 Minutes**




Semester II

Branch: **G-section**

Subject Code: EE 124

Max Marks: **20**

NOTE: All questions are compulsory. Assume the necessary data suitably if any missing.

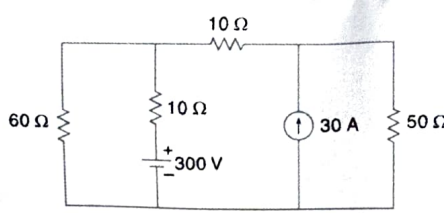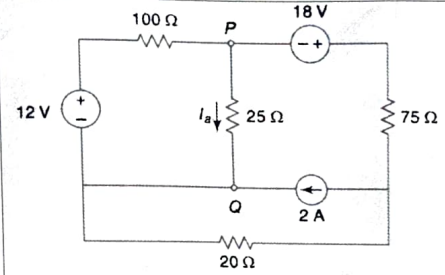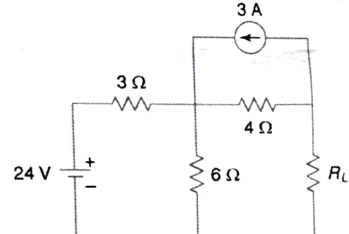Q. No.	Question	Marks
1 a.	Determine power dissipated in 60 ohms resistor.	2
		
1 b.	In the circuit shown in Fig. find current I_a using super position theorem.	3
		
2	Determine current through R_L For different values of R_L (i) $10\ \Omega$ (ii) $20\ \Omega$ and (iii) $30\ \Omega$.	4
		
3 a)	A resistance of 10 ohms is connected in series with an inductance of 0.05 H and a capacitance of 300 mF to a 100 V ac supply. Calculate the value and phase angle of the current when the frequency is (a) 25 Hz (b) 50 Hz.	3
3 b)	Three loads are placed across 230V, 50Hz supply. The loads are $10\ \angle -30^\circ\ \text{W}$; $20\ \angle 60^\circ\ \text{W}$ and $40\ \angle 0^\circ\ \text{W}$. Determine (i) the admittance (ii) equivalent impedance (iii) power consumed and (iv) power factor.	3
4	Draw the equivalent circuit diagram of the transformer referred to H.V. side. Draw the phasor diagram and determine voltage regulation expression using equivalent circuit diagram for lagging p.f. load.	5

MAULANA AZAD NATIONAL INSTITUTE OF TECHNOLOGY, BHOPAL

END TERM EXAMINATION, June 2023

B.Tech. II Semester



Subject: Basic Electrical & Electronics Engg.

Time : 3 Hours

Subject code : EE-108

Max. Marks : 50

Note: (i) Assume the necessary data suitably, if any missing.
(ii) All questions carry equal marks.

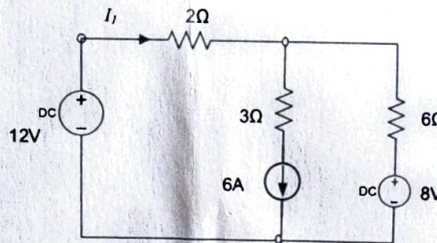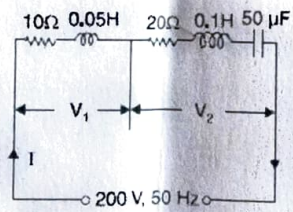Q.No.	Questions	Marks
Q.1.	<p>a) Derive the condition of maximum power transfer in any D.C. circuit and find the efficiency when the source is transferring maximum power to the load.</p> <p>b) Determine the current I_1 in the circuit of given figure using Superposition theorem.</p> 	5 5
Q.2.	<p>(a) In the given circuit, find the values of: (i) the current I (ii) V_1 and V_2 and (iii) Power factor. Draw the phasor diagram.</p>  <p>(b) Describe the phenomenon of resonance in parallel circuit and explain its Q factor. Why parallel resonance circuit is often regarded as rejector circuit?</p>	5 5
Q.3.	<p>(a) In a 50 kVA, 1100/220 V transformer, the iron and copper losses at full load are 350 W and 425 W, respectively. Calculate the efficiency at</p> <ol style="list-style-type: none"> half load with unity power factor full load with 0.8 power factor lagging and Maximum Efficiency and the load at which maximum efficiency occurs assuming the load to be resistive. <p>(b) Draw the equivalent circuit diagram of the transformer referred to secondary side. Draw the phasor diagram for this circuit and determine voltage regulation expression for lagging p.f. load.</p>	5 5

P.T.O.

Q.4.	(a) What are the main parts of D C Machine ? Write the function of each part and state the material of which each part is made?	5
	(b) Develop an expression for the speed of a d c motor in terms of back emf and flux per pole.	5
Q.5.	(a) Draw and explain V-I characteristic of P-N Junction diode when it is (i) forward biased (ii) reverse biased.	5
	(b) Derive the expression of output voltage and efficiency of full wave rectifier.	5